

Chapter 26 – Direct-Current and Circuits

- Resistors in Series and Parallel
- Kirchhoff's Rules
- Electric Measuring Instruments
- R-C Circuits

1. Resistors in Series and Parallel

Resistors in Series:

$$V_{ax} = I R_1 \quad V_{xy} = I R_2 \quad V_{yb} = I R_3$$

$$V_{ab} = V_{ax} + V_{xy} + V_{yb} = I (R_1 + R_2 + R_3)$$

$$V_{ab}/I = R_1 + R_2 + R_3 = R_{eq}$$

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$


Resistors in Parallel:

$$I_1 = V_{ab}/R_1 \quad I_2 = V_{ab}/R_2 \quad I_3 = V_{ab}/R_3$$


$$I = I_1 + I_2 + I_3 = V_{ab} (1/R_1 + 1/R_2 + 1/R_3) \rightarrow I/V_{ab} = 1/R_{eq}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$


(a) R_1 , R_2 , and R_3 in series

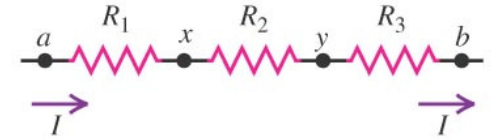


(b) R_1 , R_2 , and R_3 in parallel

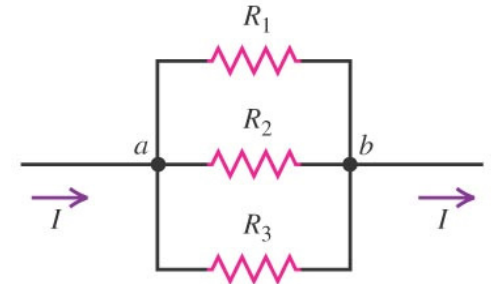

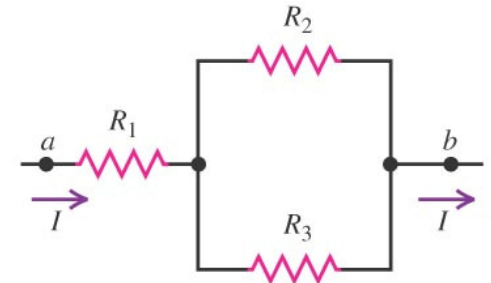(c) R_1 in series with parallel combination of R_2 and R_3



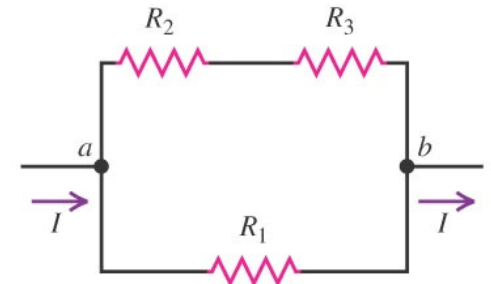(d) R_1 in parallel with series combination of R_2 and R_3






2. Kirchhoff's Rules

Junction: point where three or more conductors meet (nodes, branch points).

Loop: closed conducting path.

Kirchhoff's junction rule: the algebraic sum of the currents into any junction is zero.

$$\Sigma I = 0$$

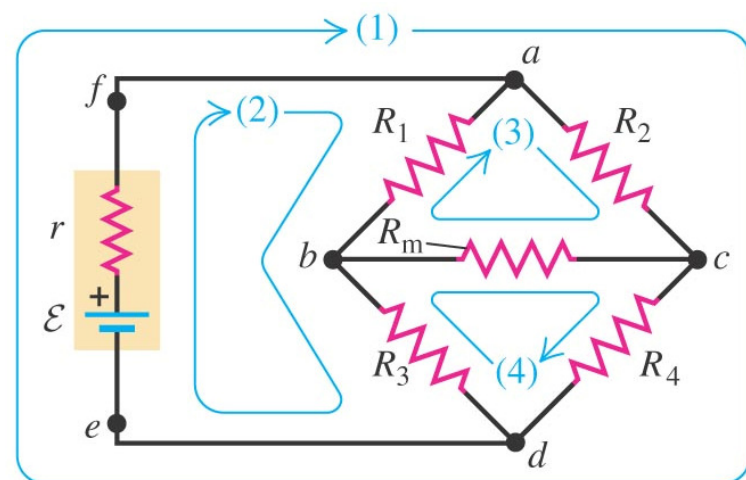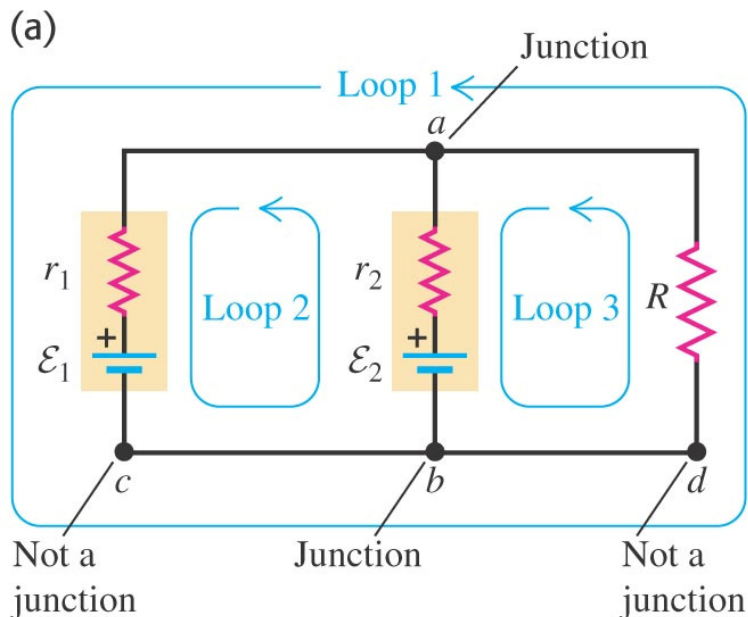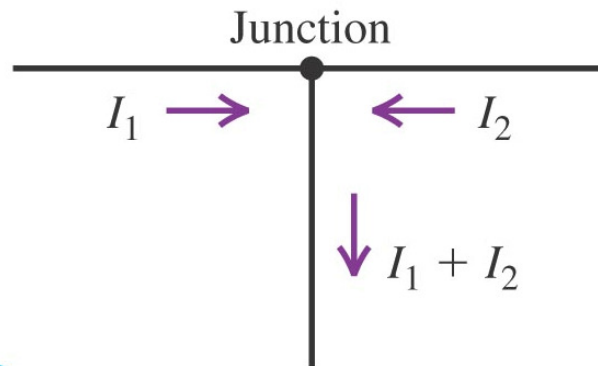

-The **junction rule is based on conservation of electric charge**. No charge can accumulate at a junction \rightarrow total charge entering the junction per unit time = total charge leaving.

Kirchhoff's loop rule: the algebraic sum of the potential difference in any loop, including those associated with emfs and those of resistive elements, must equal zero.

$$\boxed{\Sigma V = 0} \quad (\text{electrostatic force is conservative})$$

Sign Conventions for Loop Rule:


emf source (ϵ) \rightarrow positive (travel from $-$ to $+$)
negative (travel from $+$ to $-$)

resistor (IR) \rightarrow negative (travel in same direction as $I \rightarrow$ decreasing V)
positive (travel in contrary direction to $I \rightarrow$ increasing V)


- "Travel" is the direction that we imagine going around the loop, not necessarily the direction of the current.

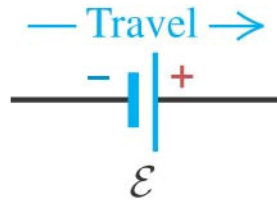(a) Sign conventions for emfs

$+\mathcal{E}$: Travel direction from $-$ to $+$:




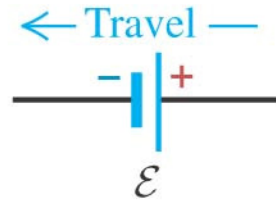$-\mathcal{E}$: Travel direction from $+$ to $-$:




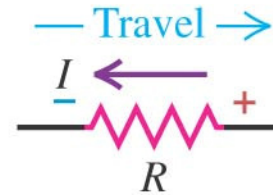(b) Sign conventions for resistors

$+IR$: Travel *opposite* to current direction:



$-IR$: Travel *in* current direction:

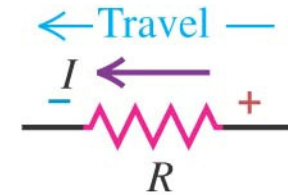

3. Electrical Measuring Instruments


d'Arsonval galvanometer (meter):

Coil of wire mounted next to a permanent magnet. Attached to the coil is a spring. Any current passing through the coil will induce magnetism in the coil (magnetic field exerts a torque on the coil \sim current). When the coil turns, spring makes restoring torque \sim angular displacement \sim current.

$$V = I_{fs} R_c$$

I_{fs} = current full scale (coil)

R_c = resistance of coil

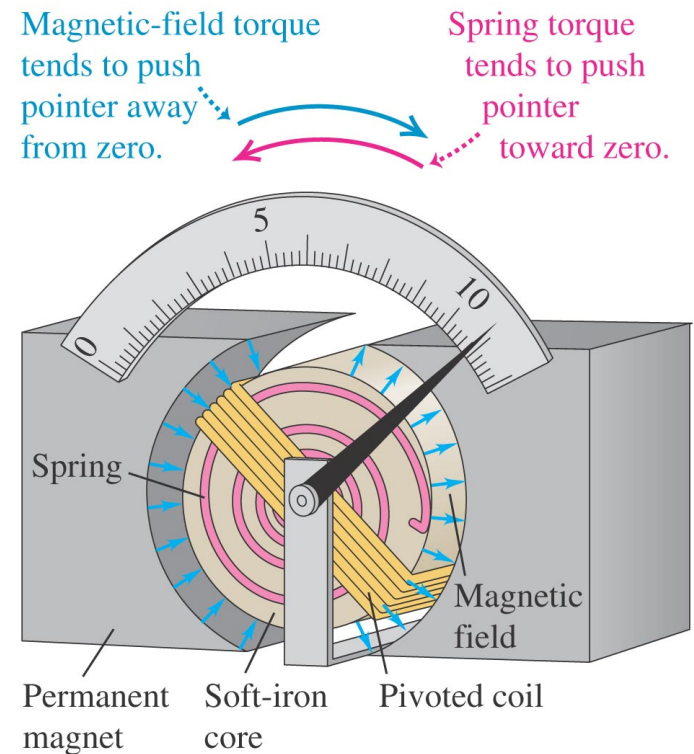

Ammeter: device that measures current, $R = 0$

- It can be adapted to measure currents larger than its full scale range by connecting R_{sh} (shunt resistor) in parallel (some I bypasses meter coil).

$$I_a = I_{sh} + I_{fs}$$

I_{fs} = current through coil

I_{sh} = current through R_{sh}



I_a = current measured by ammeter

$$V_{ab} = I_{fs} R_c = I_{sh} R_{sh} = (I_a - I_{fs}) R_{sh}$$

Voltmeter: device that measures voltage, $R = \infty$


- It can be adapted to measure voltages larger than its full scale range by connecting R_s in series with the coil .

$$V_v = V_{ab} = I_{fs} (R_c + R_s)$$

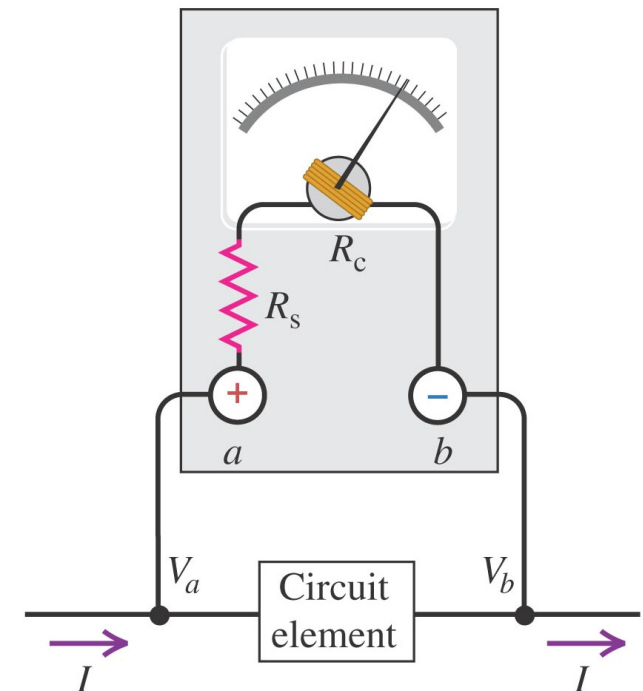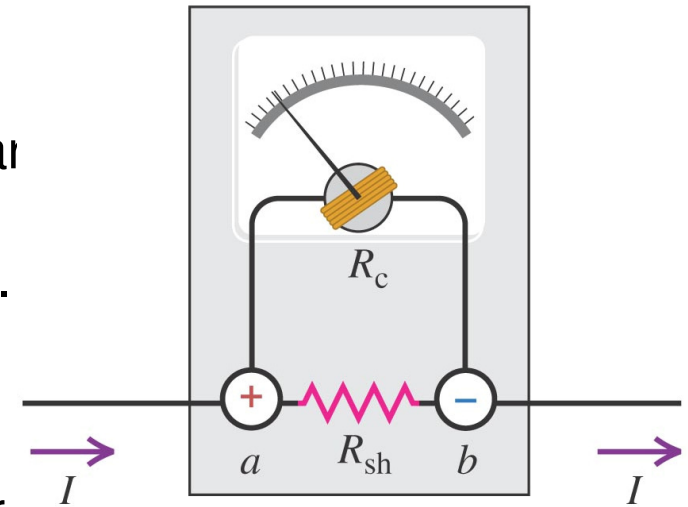

Ohmmeter: device that measures resistance.

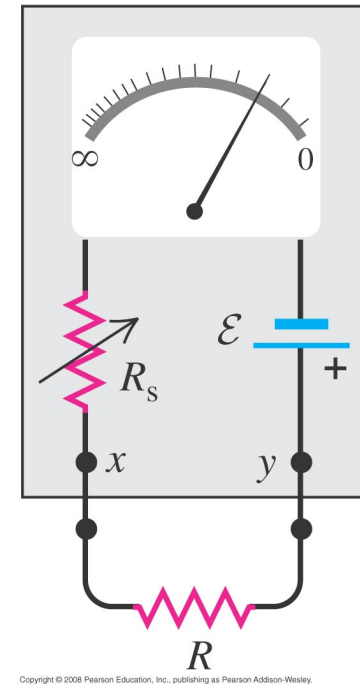
- The series resistance R_s is adjusted so that when the terminals x-y are short-circuited ($R = 0$), the meter deflects full scale (zero). When nothing is connected between x-y (open circuit, $R = \infty$) there is no current (no deflection). For intermediate R values, meter scale is calibrated to read R .



Potentiometer: device that measures emf of a source without drawing any current from it.

- R_{ab} connected to terminals of known emf (ϵ_1). A sliding contact (c) is connected through galvanometer (G) to unknown source (ϵ_2). As contact (c) is moved along R_{ab} , R_{cb} varies proportional to wire length (c-b). To find ϵ_2 (c) is moved until G shows no deflection ($I_G = 0$):

$$\epsilon = I R_{cb}$$

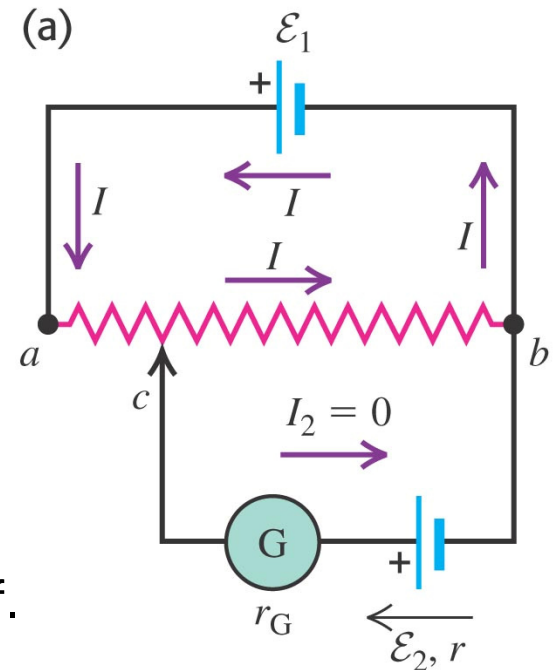

- G calibrated by replacing ϵ_2 by source of known emf.

4. R-C Circuits

- Capital letters: V, Q, I (constant)
- Lowercase letters: v, i, q (varying)

Charging a Capacitor:

$$t = 0 \rightarrow q = 0 \rightarrow v_{bc} = 0 \rightarrow I_0 = v_{ab} / R = \varepsilon / R$$

$$t = t_f \rightarrow I = 0 \rightarrow v_{ab} = 0 \rightarrow v_{bc} = \varepsilon = Q_f / C$$

At an intermediate time, t :


$$\varepsilon = v_{ab} + v_{bc}$$

$$v_{ab} = iR \quad v_{bc} = \frac{q}{C}$$


$$\varepsilon - iR - \frac{q}{C} = 0$$

$$i = \frac{\varepsilon}{R} - \frac{q}{RC} \quad \text{At } t = t_f \rightarrow i = 0 \rightarrow \frac{\varepsilon}{R} = \frac{Q_f}{RC}$$

$$Q_f = RC$$

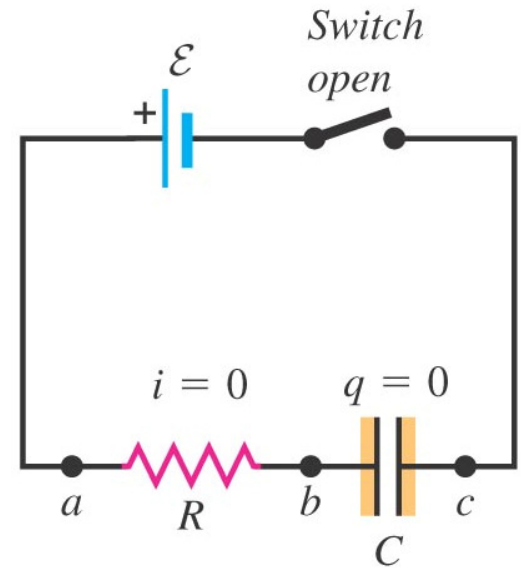

(b) Charging the capacitor

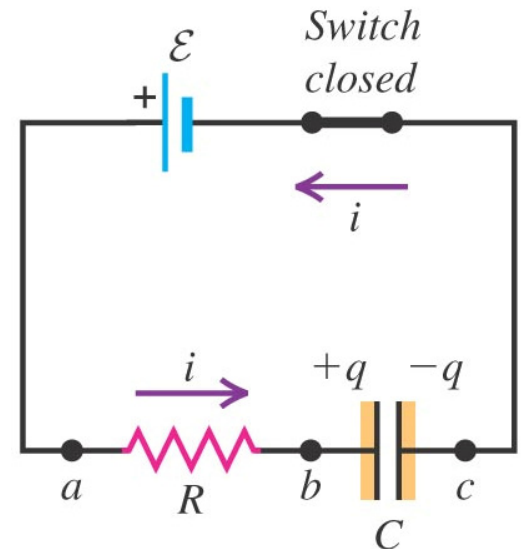

Charging a Capacitor:

$$i = \frac{dq}{dt} = \frac{\mathcal{E}}{R} - \frac{q}{RC} = -\frac{1}{RC}(q - C\mathcal{E})$$


$$\frac{dq}{q - C\mathcal{E}} = -\frac{dt}{RC}$$

$$\int_0^q \frac{dq'}{q' - C\mathcal{E}} = -\int_0^t \frac{dt'}{RC} \quad (\text{solve by changing variable } x = q' - C\mathcal{E})$$


$$\ln\left(\frac{q - C\mathcal{E}}{-C\mathcal{E}}\right) = -\frac{t}{RC} \quad \frac{q - C\mathcal{E}}{-C\mathcal{E}} = e^{-t/RC}$$

$$q = C\mathcal{E}(1 - e^{-t/RC}) = Q_f(1 - e^{-t/RC})$$
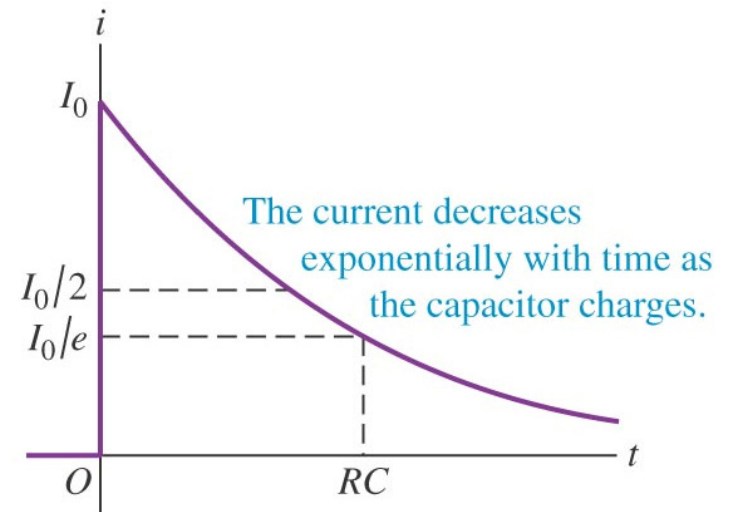
$$i = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC} = I_0 e^{-t/RC}$$



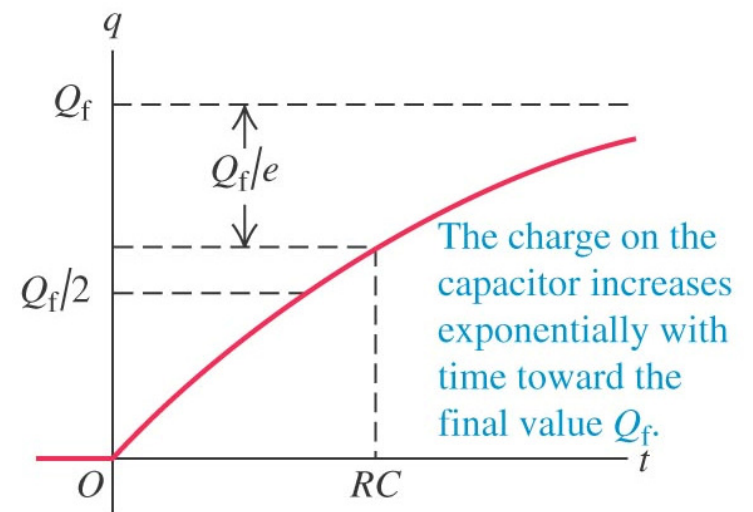(b) Graph of capacitor charge versus time for a charging capacitor



Time Constant: relaxation time of the circuit \rightarrow time after which the current in the circuit has decreased to $1/e$ of I_0 and charge has reached $(1-1/e)$ of $Q_f = C\varepsilon$.

$$\tau = RC$$

- If RC small \rightarrow circuit charges quickly.
- i never becomes exactly 0, and q never becomes exactly Q_f (asymptotic behavior).

Discharging a Capacitor:


$t = 0 \rightarrow q = Q_0$, $\varepsilon = 0$ (capacitor discharges through R)

$$-iR - \frac{q}{C} = 0$$


$$i = \frac{dq}{dt} = -\frac{q}{RC}$$

$$\int_{Q_0}^q \frac{dq'}{q'} = -\frac{1}{RC} \int_0^t dt'$$

$$\ln \frac{q}{Q_0} = -\frac{t}{RC}$$

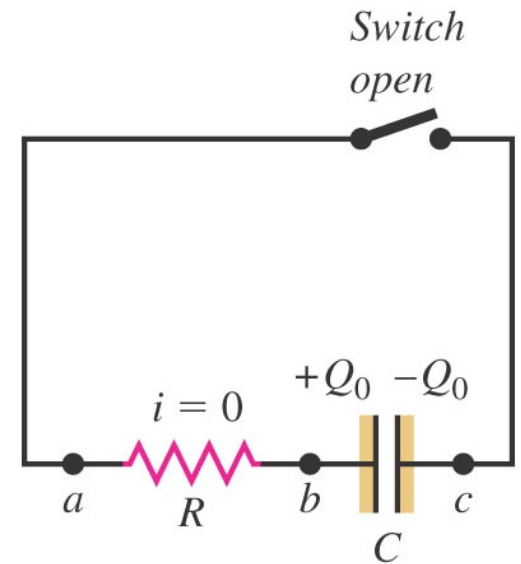


(b) Discharging the capacitor

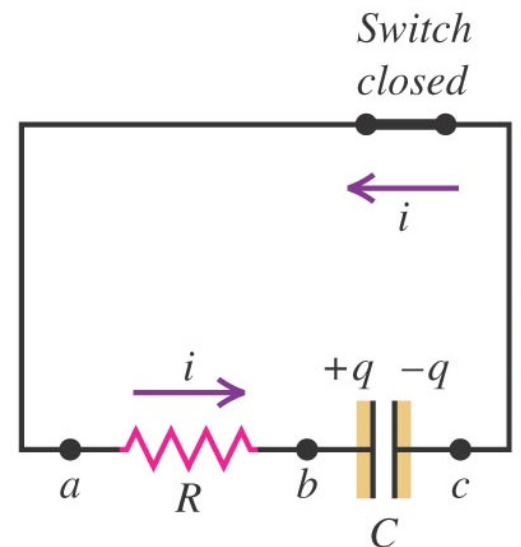

Discharging a Capacitor:

$$q = Q_0 e^{-t/RC}$$
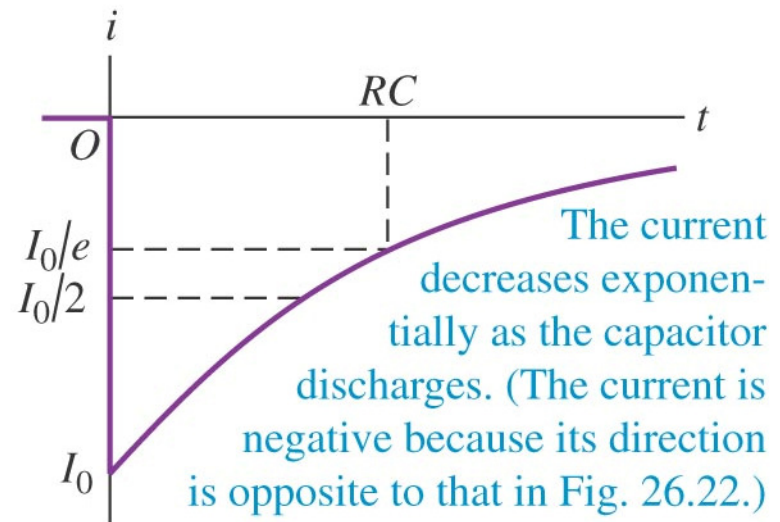
$$i = \frac{dq}{dt} = -\frac{Q_0}{RC} e^{-t/RC} = I_0 e^{-t/RC}$$



- During charging:

$$\varepsilon \cdot i = i^2 R + \frac{iq}{C}$$

Instantaneous rate at which battery delivers energy to circuit

$i^2 R$ = power dissipated in R

$i q/C$ = power stored in C

Total energy supplied by battery: εQ_f

Total energy stored in capacitor: $Q_f \varepsilon/2$

(b) Graph of capacitor charge versus time for a discharging capacitor

