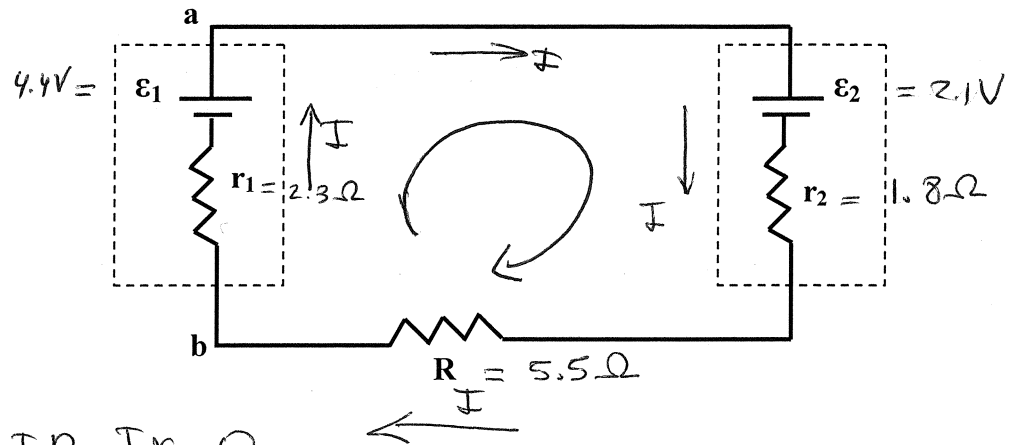


1. The electromotive force sources (emf) and resistances in the circuit below have the following values: $\epsilon_1 = 4.4 \text{ V}$, $\epsilon_2 = 2.1 \text{ V}$, $r_1 = 2.3 \Omega$, $r_2 = 1.8 \Omega$, $R = 5.5 \Omega$. r_1 and r_2 are the internal resistances of batteries 1 and 2. Calculate:

(25 points)

- (a) the current in the circuit. (8 points)
 (b) the potential difference between the terminals of battery 1. (6 points)
 (c) power dissipated by all resistors in the circuit. (6 points)



$$(a) \quad \epsilon_1 - \epsilon_2 - I r_2 - I R - I r_1 = 0$$

$$4.4 \text{ V} - 2.1 \text{ V} - I (1.8 \Omega + 2.3 \Omega + 5.5 \Omega) = 0$$

$$\boxed{I = 0.24 \text{ A}}$$

$$(b) \quad V_{ab} = V_a - V_b = \epsilon_1 - r_1 \cdot I = 4.4 \text{ V} - (2.3 \Omega)(0.24 \text{ A})$$

$$\boxed{V_{ab} = 3.8 \text{ V}}$$



$$(c) \quad P = I^2 \cdot R = I^2 (r_1 + r_2 + R) = (0.24 \text{ A})^2 (2.3 \Omega + 1.8 \Omega + 5.5 \Omega) = \boxed{0.55 \text{ W}}$$

(a) $I = 0.24 \text{ A}$	(b) $V_{ab} = 3.8 \text{ V}$	(c) $P = 0.55 \text{ W}$
--------------------------	------------------------------	--------------------------

2. (a) Find the magnitude and the direction of the current in each of the three branches of the circuit below. (15 points) (25 points)

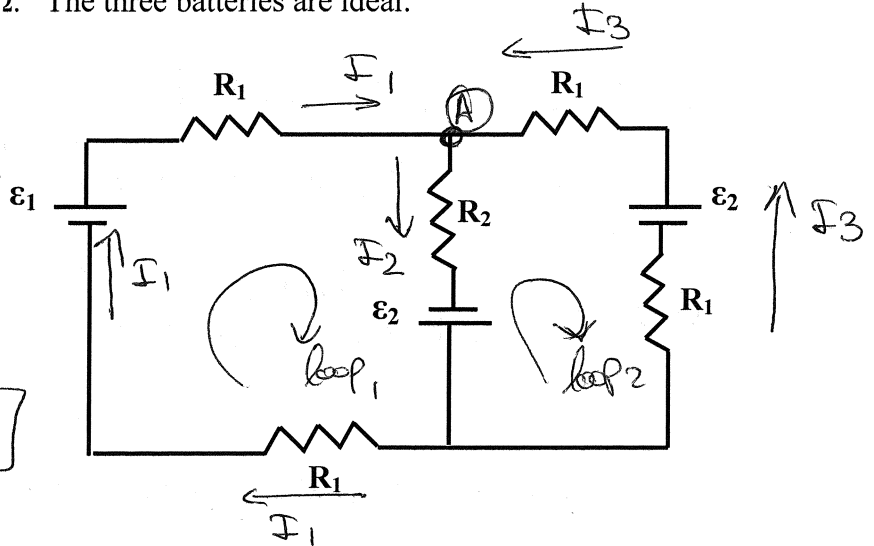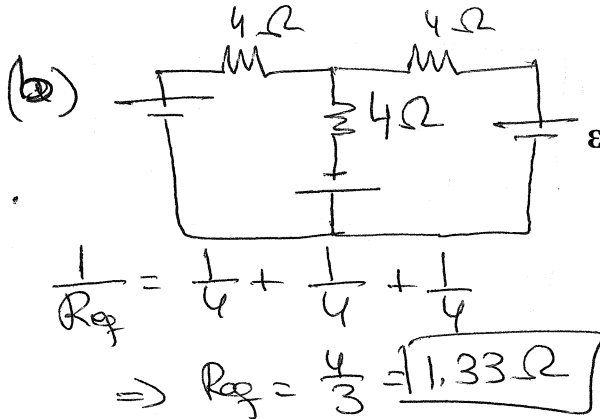(b) Find the equivalent resistance of the circuit. (15 points)

$\epsilon_1 = 3 \text{ V}$, $\epsilon_2 = 6 \text{ V}$, $R_1 = 2 \Omega$, $R_2 = 4 \Omega$. The three batteries are ideal.



(A) $I_1 + I_3 = I_2$ (1)

loop 1: $\epsilon_1 - I_1 R_1 - I_2 R_2 + \epsilon_2 - I_1 R_1 = 0 \Rightarrow 3 - 4I_1 - 4I_2 + 6 = 0$
 (2) $9 - 4I_1 - 4I_2 = 0$

loop 2: $-\epsilon_2 + R_1 I_3 - \epsilon_2 + I_2 R_2 + I_3 R_1 = 0 \Rightarrow -12 + 4I_3 + 4I_2 = 0$
 (3) $-12 + 4I_2 - 4I_1 + 4I_2 = 0$
 $-12 + 8I_2 - 4I_1 = 0$
 $+2I_1 - 12I_2 = 0 \Rightarrow I_2 = \frac{2I_1}{12} = 1.75 \text{ A}$

From (2) $9 - 4I_1 - 4I_2 = 0 \Rightarrow I_1 = \frac{+4I_2 - 9}{-4} = \frac{+4(1.75\text{A}) - 9}{-4} = 0.5 \text{ A}$

(1) $I_3 = I_2 - I_1 = 1.75 \text{ A} - 0.5 \text{ A} = 1.25 \text{ A}$

(a) $I_1 =$	$I_2 = 1.75 \text{ A}$ $I_3 =$	(b) $R_{eq} = 1.33 \Omega$
-------------	--------------------------------	----------------------------


3. Two resistors ($R_1 = 5 \text{ M}\Omega$, $R_2 = 15 \text{ M}\Omega$) are connected in series with a capacitor with capacitance $C = 2 \text{ }\mu\text{F}$ and a battery with emf $= 14 \text{ V}$. Before the switch is closed at time $t = 0$, the capacitor is uncharged. (25 points)

(a) What is the time constant of this circuit?

(b) What fraction of the final charge is on the plates of the capacitor at $t = 30 \text{ s}$?

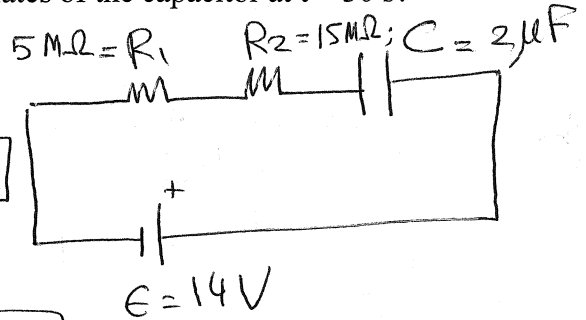(a) $R_{\text{eq}} = R_1 + R_2 = 20 \text{ M}\Omega$

$\tau = R \cdot C = (20 \text{ M}\Omega) \cdot (2 \text{ }\mu\text{F}) = \boxed{40 \text{ s}}$




(b) $\frac{q}{Q_f} = (1 - e^{-t/RC}) = 1 - e^{-30/40} = \boxed{0.53}$

Capacitor is 53% charged after $t = 30 \text{ s}$

(a) $RC = 40 \text{ s}$	(b) $q/Q_f = 0.53$
-------------------------	--------------------

4. The magnetic field B in a certain region is 0.2 T and its direction is that of the $+z$ axis in the figure below. The sides of the cube are 1.5 m long. (25 points)

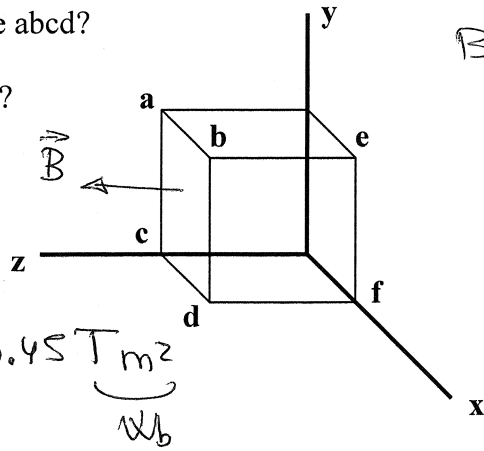- (a) What is the magnetic flux across the surface $abcd$?
 (b) What is the magnetic flux across $bedf$?
 (c) What is the net flux through all six surfaces?



$$B = 0.2\text{ T} \quad \underline{+z}$$

$$\Phi_B = B_{\perp} \cdot A = BA \cos \theta$$

(a) $\Phi_{B_{abcd}} = (0.2\text{ T}) \cdot (1.5\text{ m})^2 \cdot \cos 0^\circ = 0.45\text{ T m}^2$

(b) $\Phi_{B_{bedf}} = BA \cos 90^\circ = 0$

(c) $\Phi_{\text{TOTAL}} = 0 = BA - BA + \underbrace{0+0+0+0}_{4 \text{ surfaces}}$

(a)	(b)	(c)
-----	-----	-----