

$$V(t) = V_{MAX} e^{i\omega t}$$

$$V(t) - L \frac{dI}{dt} = 0$$

$$V_{MAX} e^{i\omega t} - L \frac{dI}{dt} = 0$$

$$V_{MAX} e^{i\omega t} = L \frac{dI}{dt}$$

$$\frac{dI}{dt} = \frac{V_{MAX}}{L} e^{i\omega t}$$

$$I(t) = \frac{V_{MAX}}{i\omega L} e^{i\omega t}$$

$$i^2 = -1$$

$$I(t) = -\frac{i V_{MAX}}{\omega L} e^{i\omega t}$$

$$I(t) = \frac{V_{MAX}}{\omega L} e^{i\omega t - i\pi/2}$$

$$I(t) = \frac{V_{MAX}}{\omega L} e^{i(\omega t - \pi/2)}$$


$$e^{i\theta} = \cos\theta + i\sin\theta$$

$$-i = e^{-i\pi/2}$$

COMPLEX IMPEDANCE

$$Z_L = i\omega L$$

EXAMPLE

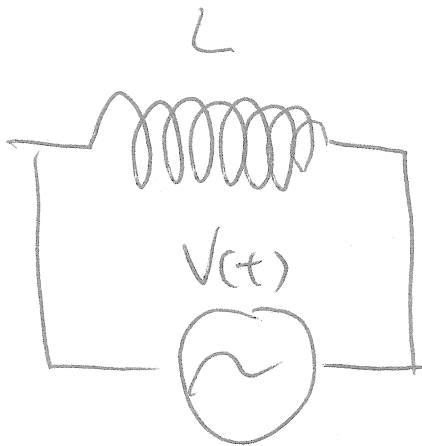

GIVEN $V(t)$


WHAT IS $I(t)$

$$V(t) = I(t) Z_{\text{TOTAL}}$$

$$V(t) = I(t) i\omega L$$


$$I(t) = \frac{V(t)}{i\omega L} = -i \frac{V(t)}{\omega L}$$
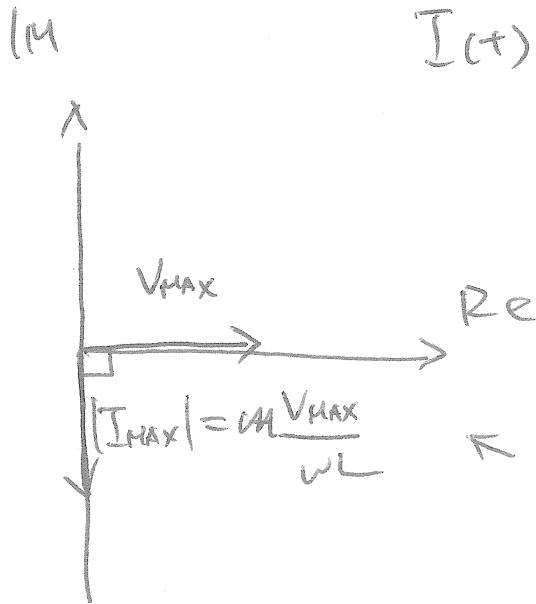
$$I_{\text{MAX}} e^{i\omega t} = \underbrace{-\frac{i}{\omega L}}_{\text{}} V_{\text{MAX}} e^{i\omega t}$$



CURRENT LAGS VOLTAGE BY 90°

"RLC" CIRCUIT

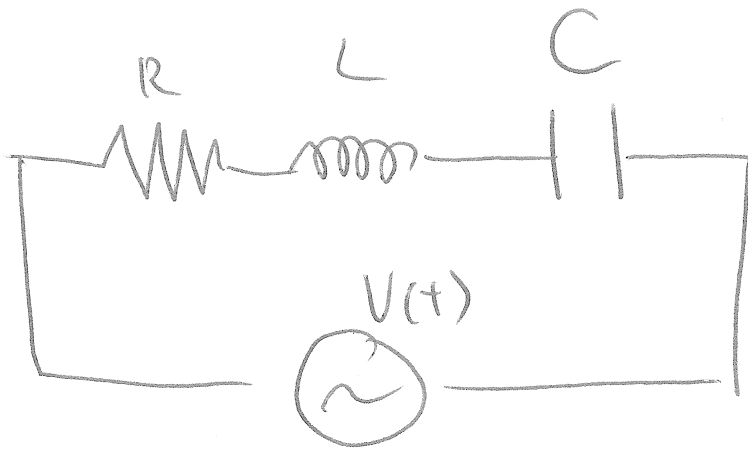

$$Z_{\text{TOTAL}} = R + i\omega L + \frac{1}{i\omega C}$$

$$Z_{\text{REAL}} = R + i\left(\omega L - \frac{1}{\omega C}\right)$$

WHAT'S THE MAGNITUDE OF COMPLEX IMPEDANCE


$$|Z_{\text{TOTAL}}| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\underline{I(t)} \stackrel{?}{\leftarrow} \underline{V(t)} \quad I(t) = \frac{V(t)}{Z_{\text{TOTAL}}}$$

$$= \frac{V(t)}{R + i\left(\omega L - \frac{1}{\omega C}\right)}$$

$$= \frac{V(t)}{R + i\left(\omega L - \frac{1}{\omega C}\right)} \times \frac{R - i\left(\omega L - \frac{1}{\omega C}\right)}{R - i\left(\omega L - \frac{1}{\omega C}\right)}$$

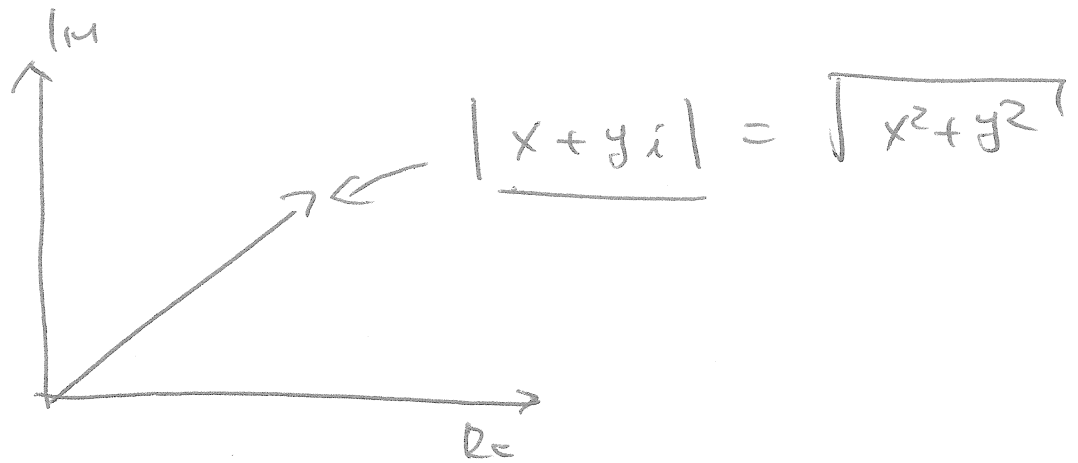
$$\underline{I(t)} = \frac{V(t) \left[R - i\left(\omega L - \frac{1}{\omega C}\right) \right]}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$



$$|I(t)| = \frac{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}{\left(R^2 + (\omega L - \frac{1}{\omega C})^2\right)^2} |V(t)|$$

$$I_{MAX} = \frac{1}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} V_{MAX}$$
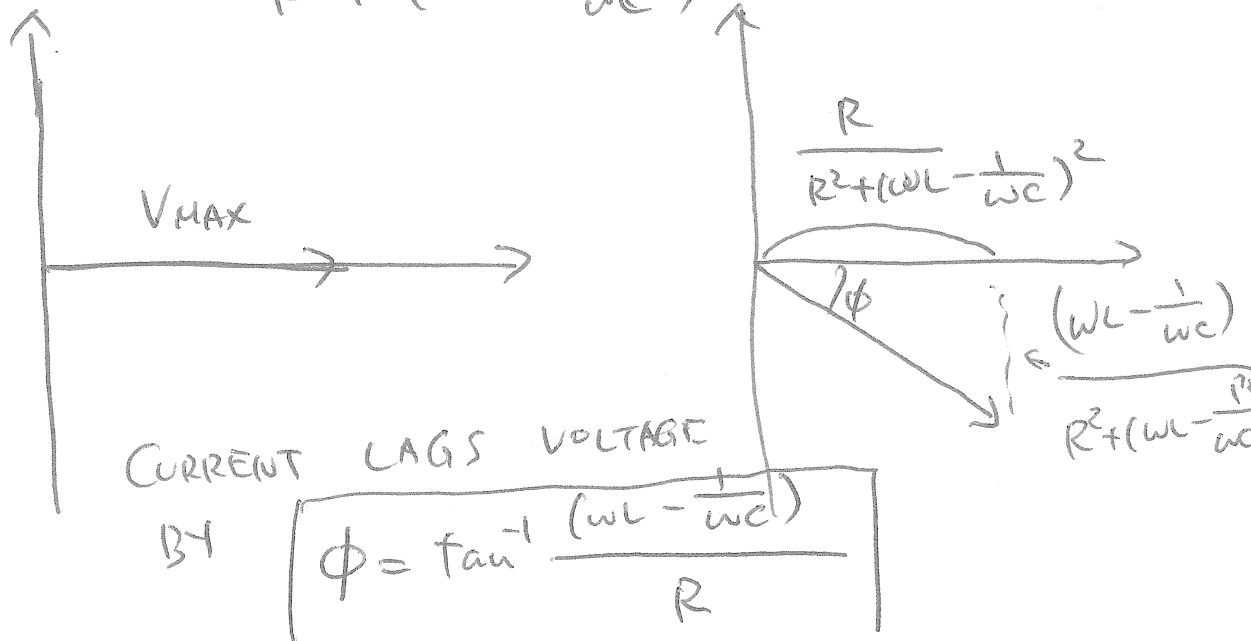
$$I(t) = \frac{V(t) \left[R - i \left(\omega L - \frac{1}{\omega C} \right) \right]}{R^2 + (\omega L - \frac{1}{\omega C})^2}$$



POWER DELIVERED TO THE CIRCUIT

$$P = IV$$

$$I = \frac{V}{Z_{\text{TOTAL}}}$$

$$P = \frac{V^2}{Z_{\text{TOTAL}}}$$

$$P = \frac{V^2}{|Z_{\text{TOTAL}}|}$$

$$P_{\text{MAX}} = \frac{V_{\text{MAX}}^2}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$