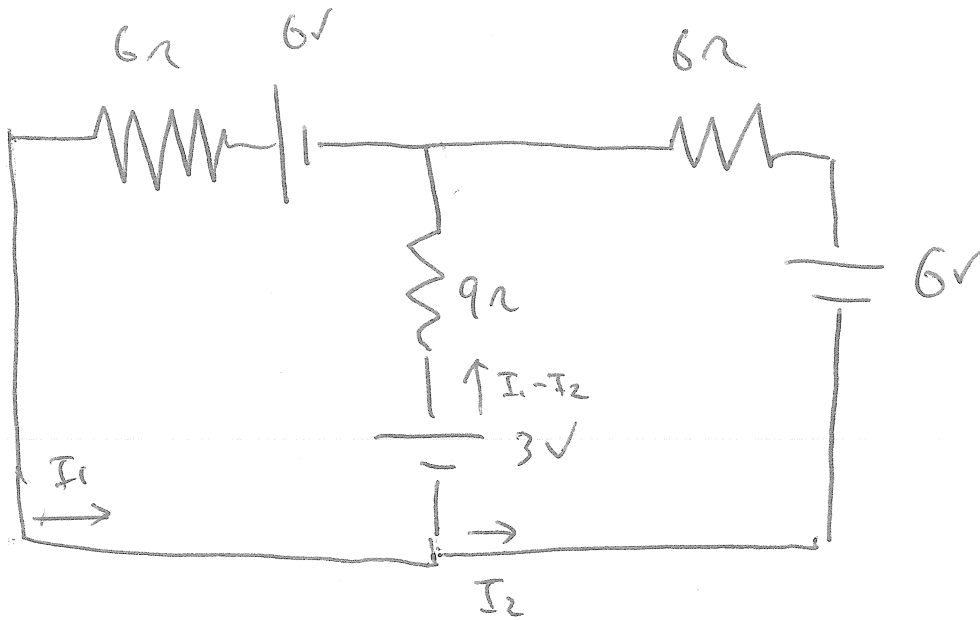


#1



CALCULATE I_1 AND I_2 .

$$3 - 9(I_1 - I_2) + 6 - 6I_1 = 0$$

$$9 - 9I_1 + 9I_2 - 6I_1 = 0$$

$$\boxed{9 - 15I_1 + 9I_2 = 0} \dots (1)$$

$$6 - 6I_2 + 9(I_1 - I_2) - 3 = 0$$

$$\boxed{3 + 9I_1 - 15I_2 = 0} \dots (2)$$

$$\boxed{I_2 = \frac{7}{8} A}$$


$$3 + 9I_1 - 15 \frac{7}{8} = 0$$

$$9I_1 = \frac{105}{8} - \frac{24}{8}$$

$$9I_1 = \frac{81}{8}$$

$$\boxed{I_1 = \frac{9}{8} A}$$

#2

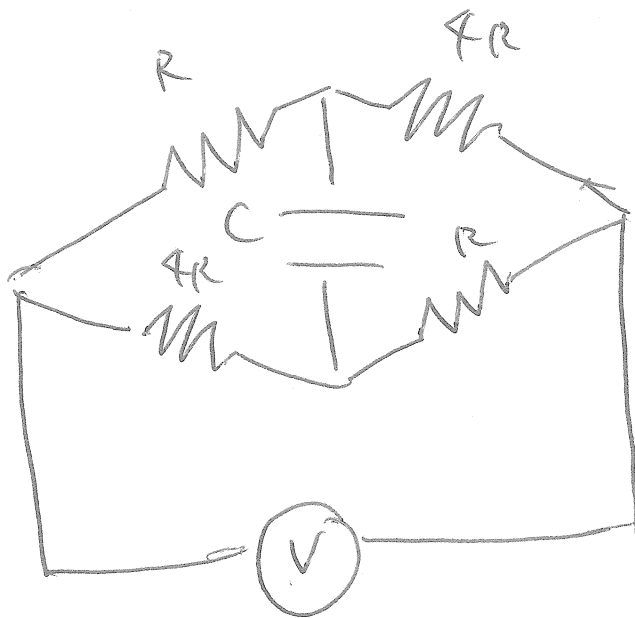

CALCULATE


a) ~~FOR~~ TOTAL CURRENT
THRU THE CIRCUIT
AT $t=0$

b) CALCULATE CHARGE ON CAPACITOR
AT $t=\infty$

$$Q = C V_c$$

At $t=0$

$$Q=0 \quad V_c=0$$

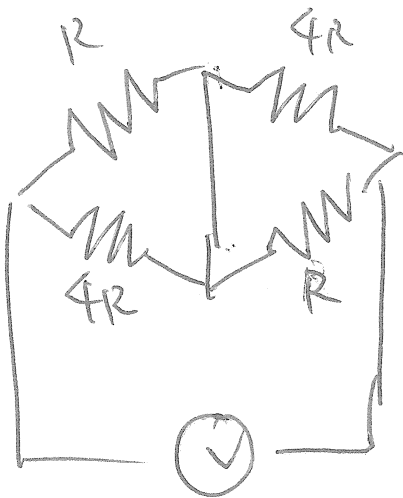


a) $\frac{1}{R} + \frac{1}{4R} = \frac{5}{4R} \Rightarrow \frac{4R}{5}$

\therefore ~~SECS~~ $R_{TOTAL} = \frac{8R}{5}$


$$V = I R_{TOTAL}$$

$$V = I \frac{8R}{5}$$

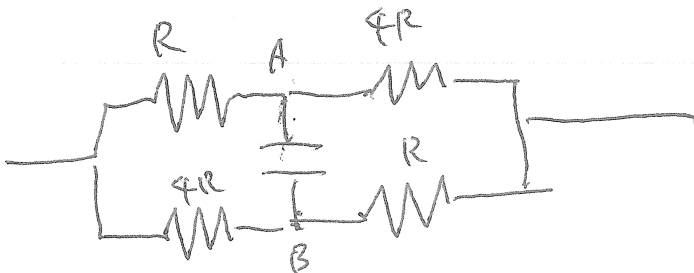
$$I = \frac{V \cdot 5}{8R} = \frac{5V}{8R}$$



$$V_A - V_B = 0$$

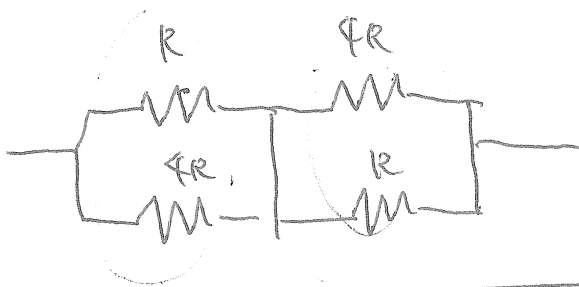

$\leftarrow T=0$

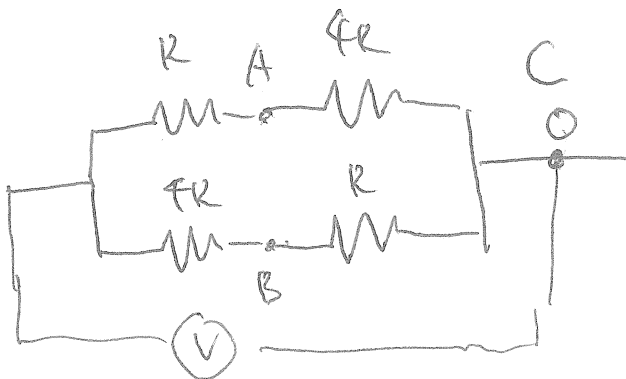

$$V_A - V_B$$

~~R_{total} = 5R~~

$$\frac{1}{5R} + \frac{1}{5R} = \frac{1}{R_{\text{total}}}$$

$$\frac{2}{5R} = \frac{1}{R_{\text{total}}}$$

$$R_{\text{total}} = R_{\text{in}} = \frac{5R}{2}$$

$$I_{\text{total}} = \frac{2V}{5R}$$

CURRENT THRU TOP AND BOTTOM

$\frac{V}{5R}$ EACH

$$V_A - V_C = \frac{4}{5}V$$



$$V_A - V_B = \frac{3}{5}V$$


$$V_B - V_C = \frac{1}{5}V$$

$$Q = CV$$

$$Q = \frac{3}{5}CV$$

I_{INDUCED}

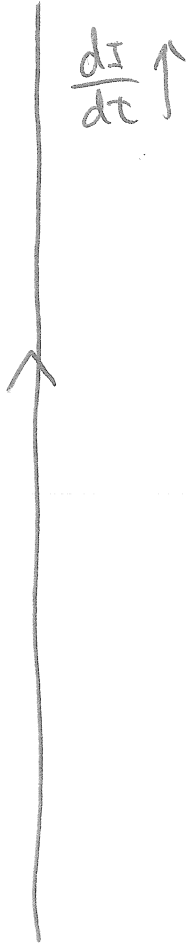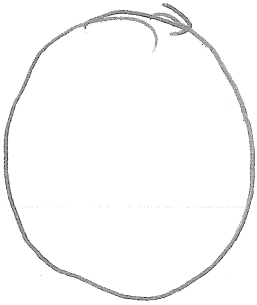


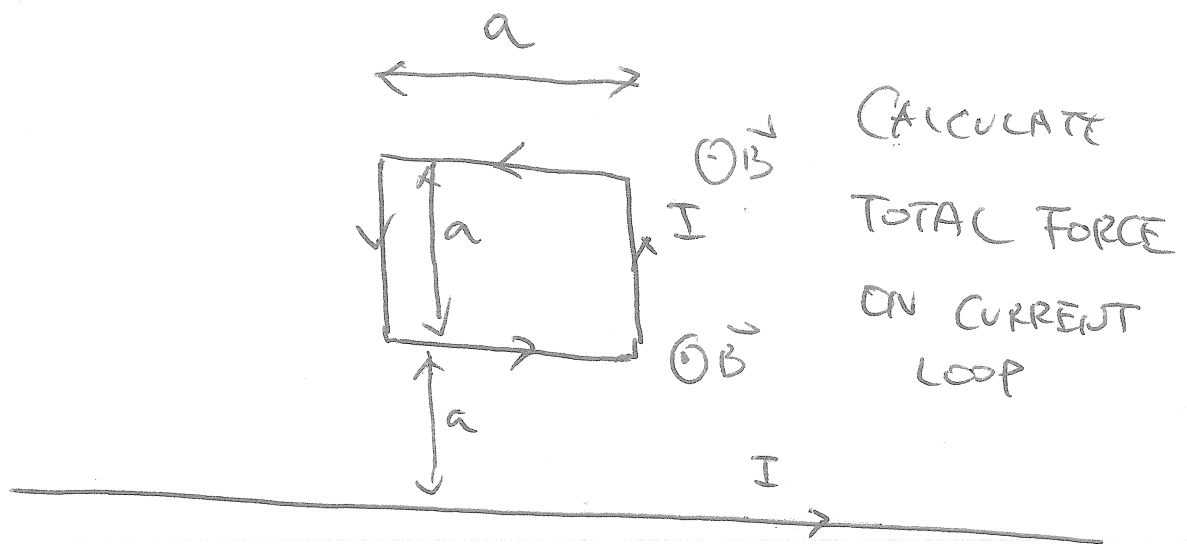

$$\oint \vec{B} \cdot d\vec{s} = \mu_0 I$$

$$B \cdot 2\pi r = \mu_0 I \Rightarrow B = \frac{\mu_0 I}{2\pi r}$$

$$\vec{F} = I \vec{L} \times \vec{B}$$

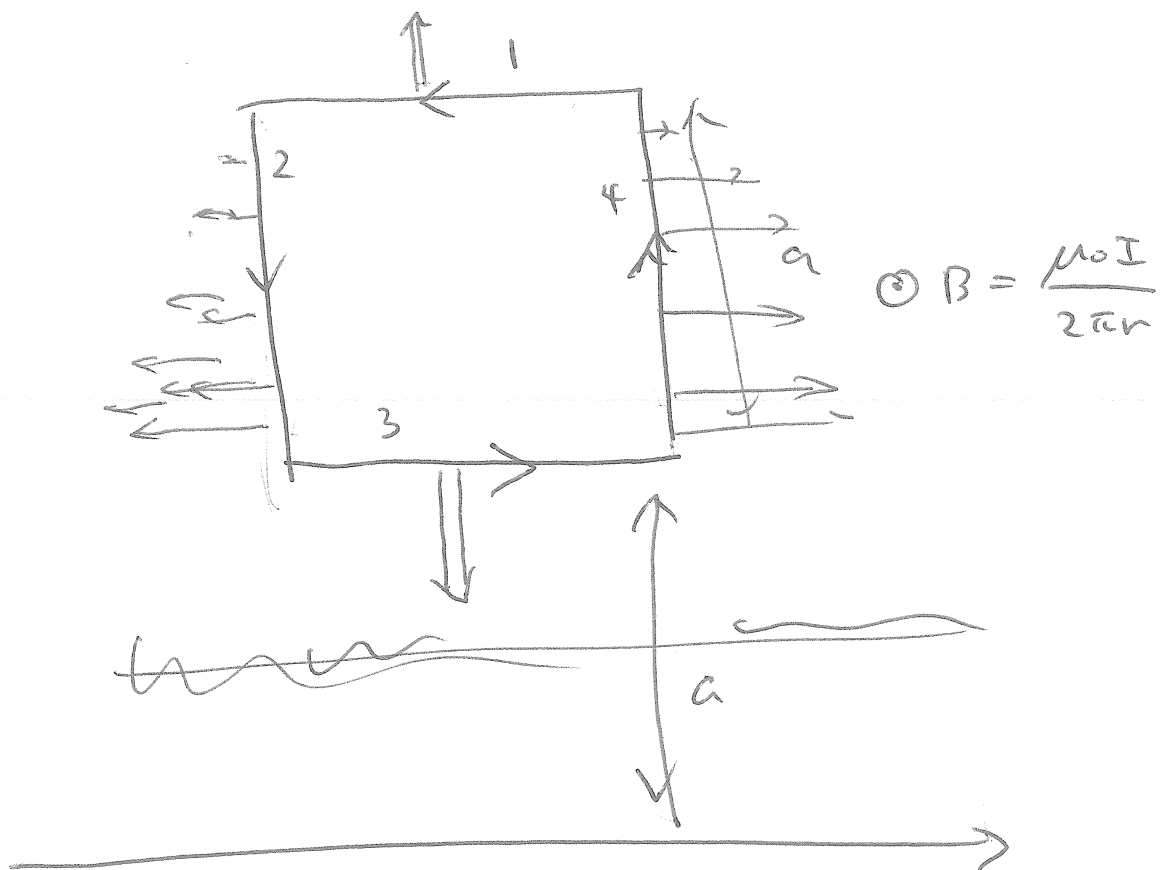

$$\vec{F}_2 + \vec{F}_4 = 0$$

$$|\vec{F}_3| = |I \vec{L} \times \vec{B}|$$


$$= I \frac{\mu_0 I}{2\pi a} \cdot a$$

$$= \frac{\mu_0 I^2}{2\pi}$$

$$|\vec{F}_1| = I \frac{\mu_0 I}{4\pi a} \cdot a = \frac{\mu_0 I^2}{4\pi}$$

$$|\vec{F}_{\text{TOTAL}}| = \frac{\mu_0 I^2}{4\pi} \quad \text{POINTING IN}$$

TOWARDS
THE OTHER WIRE

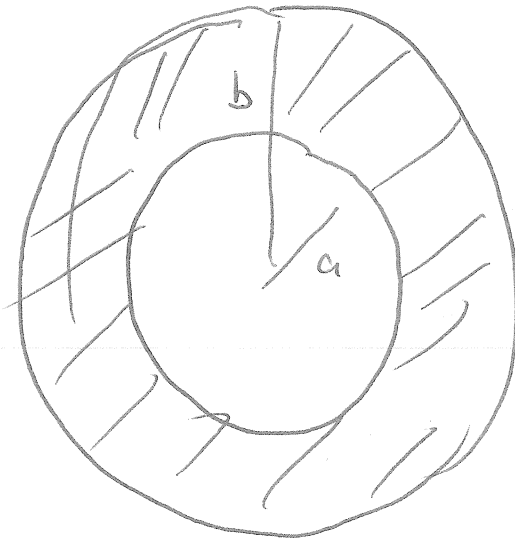

TOTAL CURRENT I


CALCULATE \vec{B}

FOR $a < r < b$

UNIFORM CURRENT DENSITY

CURRENT DENSITY

$$\frac{I}{\pi(b^2 - a^2)}$$

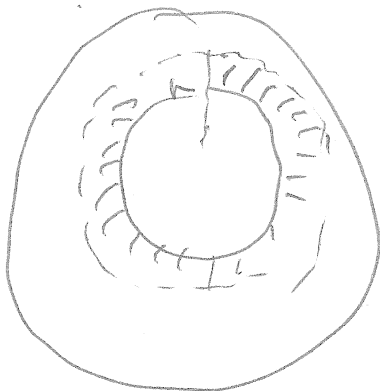

$$\oint \vec{B} \cdot d\vec{S} = B \cdot 2\pi r = \mu_0 I_{enc}$$

$$B \cdot 2\pi r = \mu_0 I \frac{\pi(r^2 - a^2)}{\pi(b^2 - a^2)}$$

$$= \frac{\mu_0 I \pi (r^2 - a^2)}{\pi (b^2 - a^2)}$$