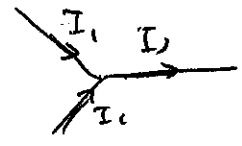


LECTURE 4/28/23


KIRCHHOFF'S RULES

KIRCHHOFF'S RULE.

1. CONSERVATION OF CHARGE





2. CONSERVATION OF ENERGY

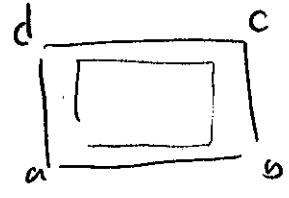

$$\sum_{\text{CLOSED LOOP}} \Delta V = 0$$

2. EASY EXAMPLE

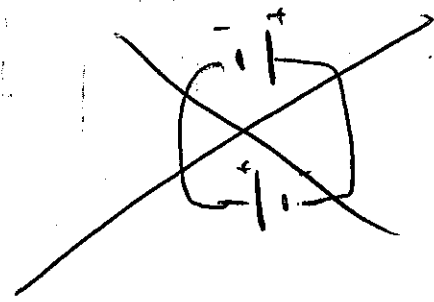

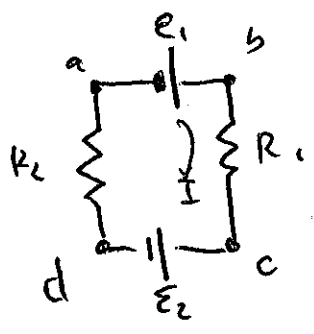


$$\sum \Delta V = 0$$

- a → b +E₁
- b → c -IR₁
- c → d -E₂
- d → a -IR₂

$$E_1 - IR_1 - E_2 - IR_2 = 0$$

~~IF EXAMPLE ALSO TAKE~~


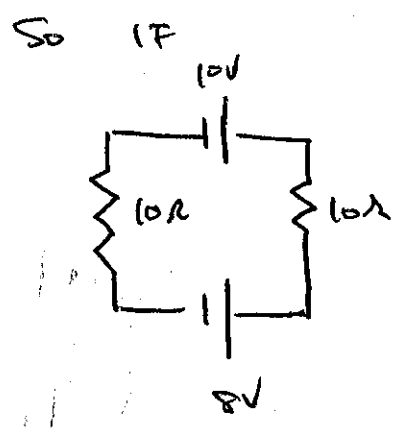


$$10V - I10\Omega - 8V - I10\Omega = 0$$

$$2V = I20\Omega$$

$$\boxed{\frac{1}{10} A = I}$$


EXAMPLE 2

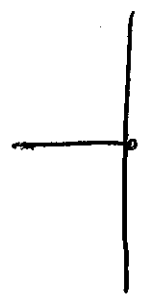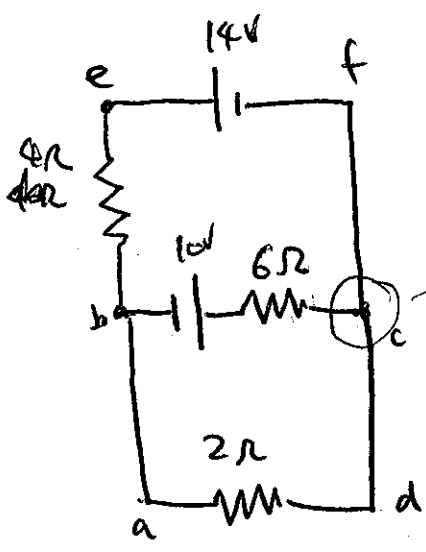

FIND CURRENTS


WALK THROUGH THIS ONE REALLY

CLOSED LOOPS

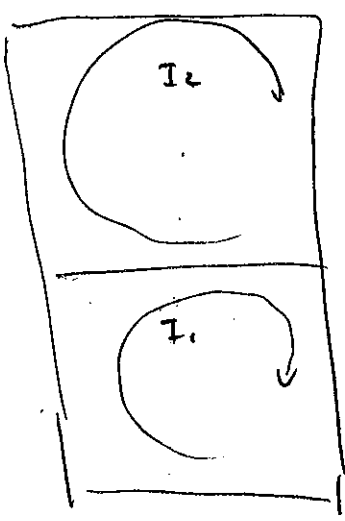

abcd: a → b 0
 b → c ~~10V - 6R(I1 - I2)~~
 e → d 0
 d → a - I1 2R
 befc: b → e ~~4R - 4R I2~~
 e → f - 14V
 f → c 0
 c → b - I2 6R - 10V

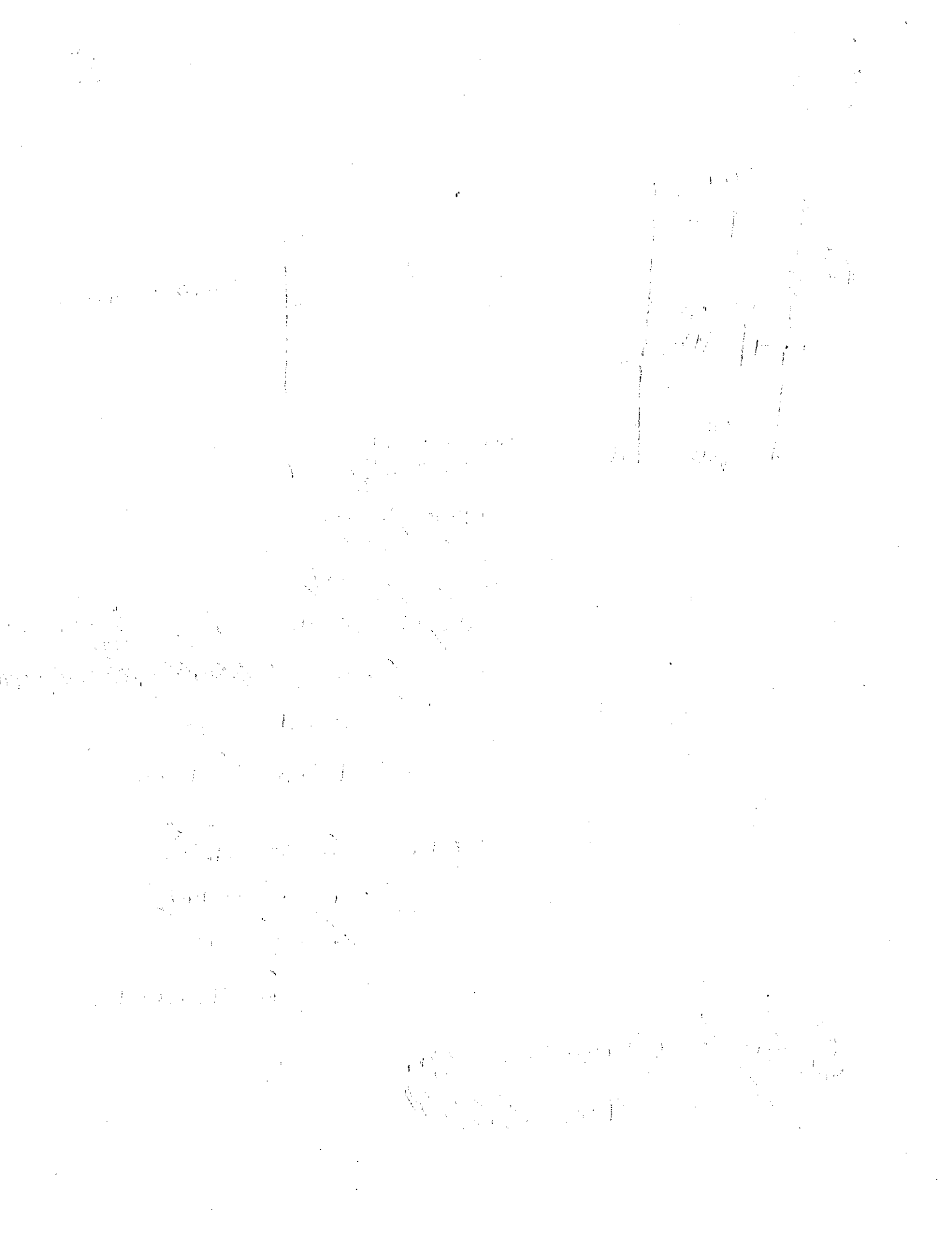~~$$I_1 \cdot 2R = 0 + 10V - 6I_1 - 2I_1 I_1$$~~
~~$$10V + 8I_1 = 0$$~~



$$\begin{array}{r} I_1 - I_2 \\ \hline I_2 \\ \hline I_1 \end{array}$$

14
13
12

$$15I_1 - 10V - 6(I_1 - I_2) - 2I_1 = 0$$

$$10V - 6I_1 + 6I_2 - 2I_1 = 0$$

$$8I_1 - 6I_2 = 10V$$

~~$$-8I_1 + 6I_2 = -10V$$~~

2nd loop

$$-4I_2 - 14 - 6(I_2 - I_1) - 10V = 0$$

$$-10I_2 + 6I_1 = 24$$

~~$$8I_1 - 6I_2 = 10V$$~~

~~$$-10I_2 + 6I_1 = 24$$~~ $\times \frac{4}{3}$

$$8I_1 - 6I_2 = 10V$$

$$- \frac{40}{3} I_2 + 8I_1 = 32$$

$$\left(-6 + \frac{40}{3}\right) I_2 = -22V$$

$$\frac{22}{3} I_2 = -22V$$


$$I_2 = -3A$$

~~14~~

POT INTO 2)

$$+30 \text{ V} = 6 I_1 = 24$$

$$I_1 = -1 \text{ A}$$

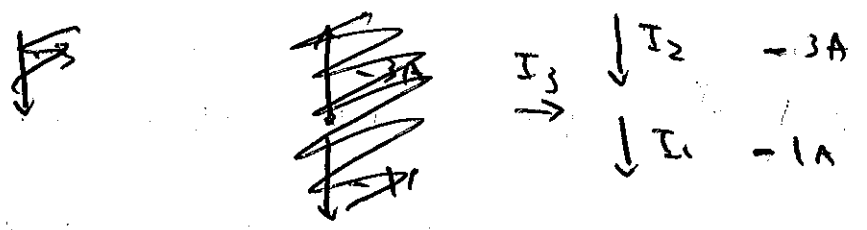


$$I_2 + I_3 = I_1$$

$$-3 \text{ A} + I_3 = -1 \text{ A}$$

$$\underline{I_3 = 2 \text{ A}}$$

CAPACITORS How??

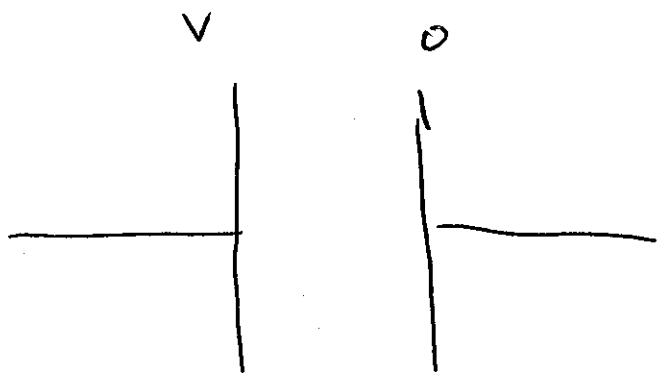


$$\Delta V = \frac{Q}{C}$$



$$\Delta V = -\frac{Q}{C}$$

RC CIRCUITS

CAPACITOR

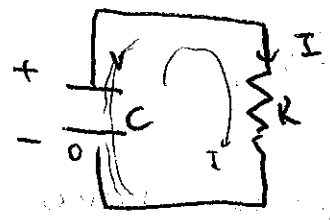

$V(t)$ $Q(t)$

$$\frac{dq}{dt} = I(t)$$

$$I = \frac{V(t)}{R}$$

$$Q = CV$$


$$C \frac{dV}{dt} = \frac{V(t)}{R}$$

$$\frac{dV}{dt} = \frac{V}{RC}$$


$$\frac{dV}{V} = \frac{dt}{RC}$$

$$\int \frac{dV}{V} =$$

$$V(t) = e^{-t/RC}$$

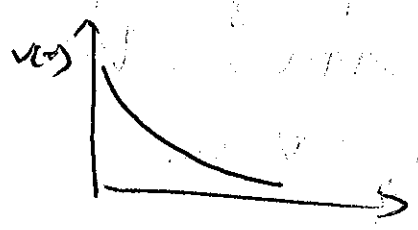

EXAMPLE

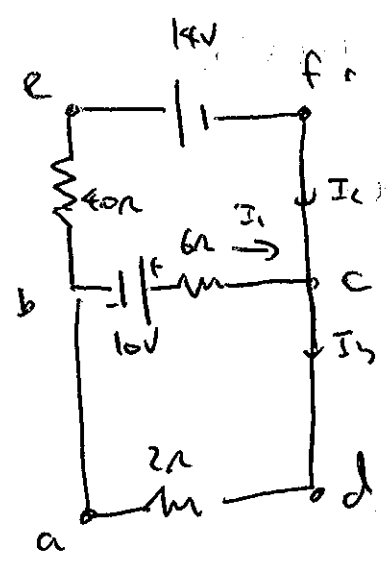

FIND I_1, I_2, I_3


$I_1 + I_2 - I_3 = 0$ KIRCHOFF'S LAW.


FOR SET UP SEE P5

$abcda = 0 + 10V - I_1 \cdot 6\Omega - I_3 \cdot 2\Omega = 0$

$befcb = -I_2 \cdot 10V + 6I_1 - 10V = 0$

SUPER POSITION LIVES

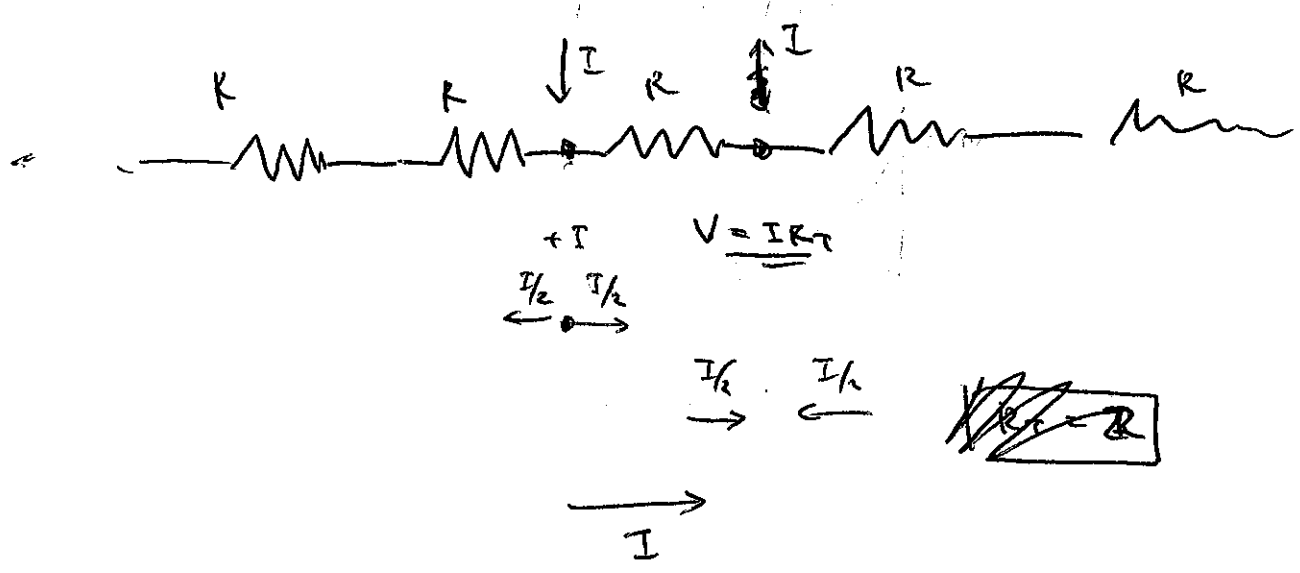

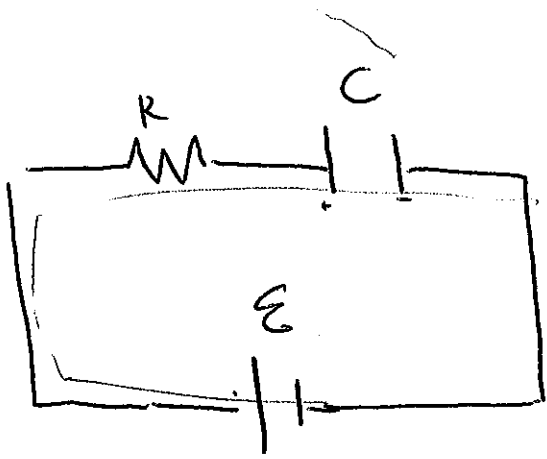

KIRCHHOFF'S LAW

$$\epsilon - \cancel{IR} - \frac{q}{C} = 0$$


$$\epsilon - \frac{dq}{dt}R - \frac{q}{C} = 0$$

$$\frac{dq}{dt} = \frac{\epsilon}{R} - \frac{q}{RC}$$

$$= \frac{\epsilon C - q}{RC}$$

$$q(t) = C\epsilon (1 - e^{-t/RC})$$

$$\tau = RC$$

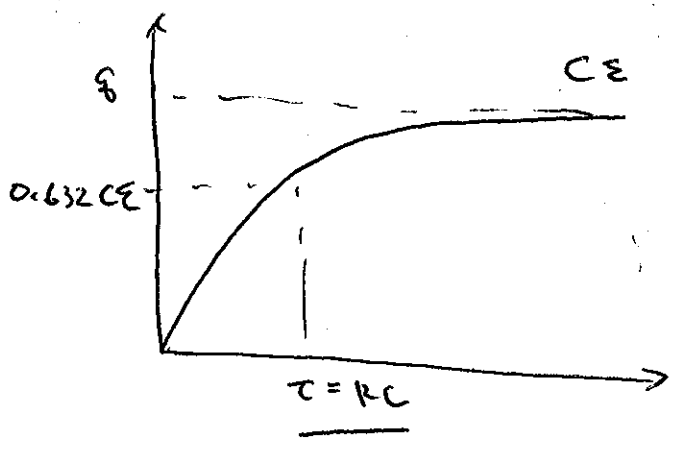

τ, RC

$\frac{dQ}{dt} = \frac{Q}{RC}$
 $\frac{dQ}{Q} = \frac{dt}{RC}$
 $\ln Q = \frac{t}{RC} + \ln C$
 $Q = C e^{\frac{t}{RC}}$

MONDAY EM 367 OHM'S LAW

WED EM 373 LIGHT BULBS, EM 361 HAND BATTERY

FRIDAY EM §-382 DISCHARGE THRU A VOLTMETER