


FINISH DISCUSSION ON RESISTIVITY FIRST

EXAMPLE

RESISTANCE ~~OF~~ PER UNIT LENGTH
 CALCULATING RESISTIVITY OF A NICHROME WIRE WITH ~~DIAMETER~~ RADIUS OF 1 mm

NICHROME WIRE
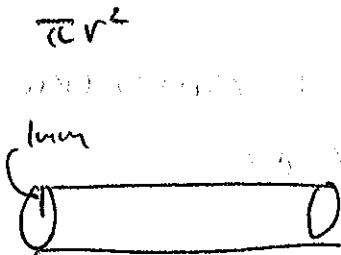
$$\rho = 1.5 \times 10^{-6} \Omega \cdot \text{m}$$



$$A = \pi r^2$$

$$= \pi (1 \times 10^{-3})^2$$

$$= 3.14 \times 10^{-6} \text{ m}^2$$

$$R = \frac{\rho l}{A} \Rightarrow$$

$$R/l = \frac{\rho}{A} = \frac{1.5 \times 10^{-6} \Omega \cdot \text{m}}{3.14 \times 10^{-6} \text{ m}^2}$$

$$\approx \underline{\underline{0.5 \Omega / \text{m}}}$$

IF 10V IS APPLIED ACROSS NICHROME WIRE THAT IS
1m LENGTH



$$V = IR$$

$$10 = 0.5 I$$

$$I = 20A$$

RESISTIVITY OF CONCENTRIC

CABLE

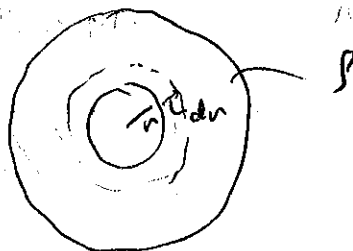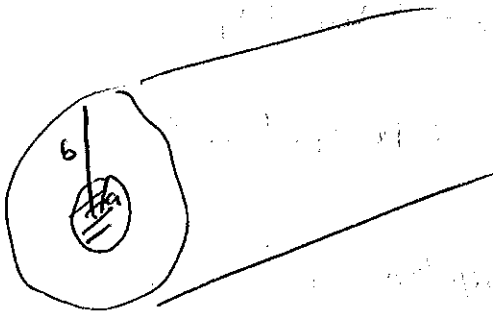

$$R = \frac{\rho l}{A}$$

$$= \frac{\rho dr}{2\pi r}$$

$$R = \frac{\rho}{2\pi} \int_a^b \frac{dr}{r}$$

$$= \frac{\rho}{2\pi} \ln r \Big|_a^b$$

$$= \frac{\rho}{2\pi} \ln \frac{b}{a}$$

MODEL FOR CONDUCTION

$$\vec{J} = \sigma \vec{E}$$

\vec{J} = CURRENT / UNIT AREA

CURRENT = $n e \cdot v_{drift}$

$\vec{F} = e \vec{E}$ SO IT SPEEDS UP

$ma = e \vec{E}$

$a = \frac{e E}{m}$ IF IT GOES FOR τ BEFORE SCATTERING COMPLETELY STOPPED

$\vec{v}_d = \frac{e E}{m} \tau$


$\vec{J} = n e \frac{e E}{m} \tau$

$\vec{J} = \frac{n e^2 \tau}{m} \vec{E}$


$$\sigma = \frac{n e^2 \tau}{m}$$

DRUDE MODEL

RESISTANCE AND TEMPERATURE

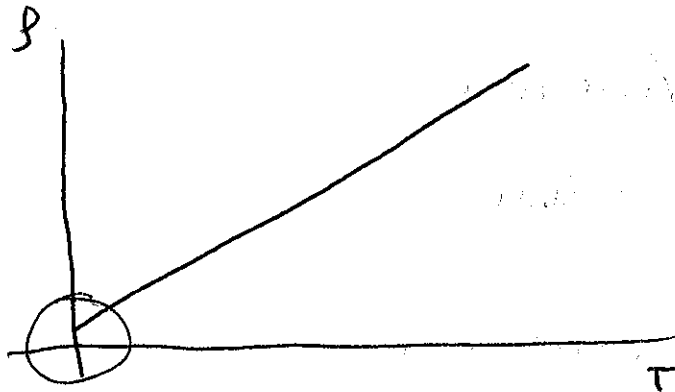

IF

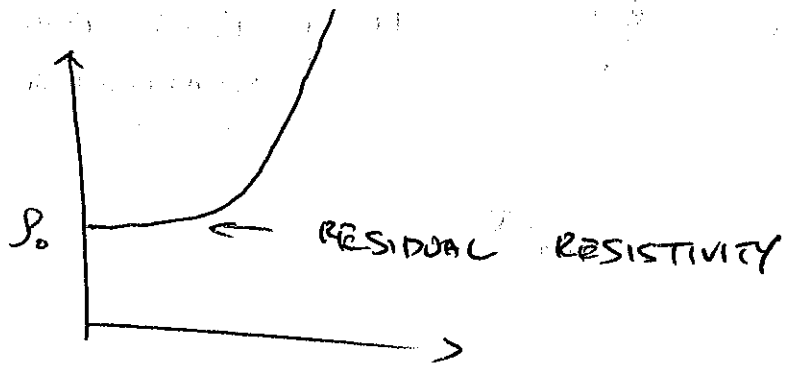

$$\text{IF } \frac{d\rho}{dT} \geq 0$$


METAL

$$\frac{d\rho}{dT} < 0$$

SEMICONDUCTOR

SUPER CONDUCTORS

1911 HEIKE KAMERLING-ONNES

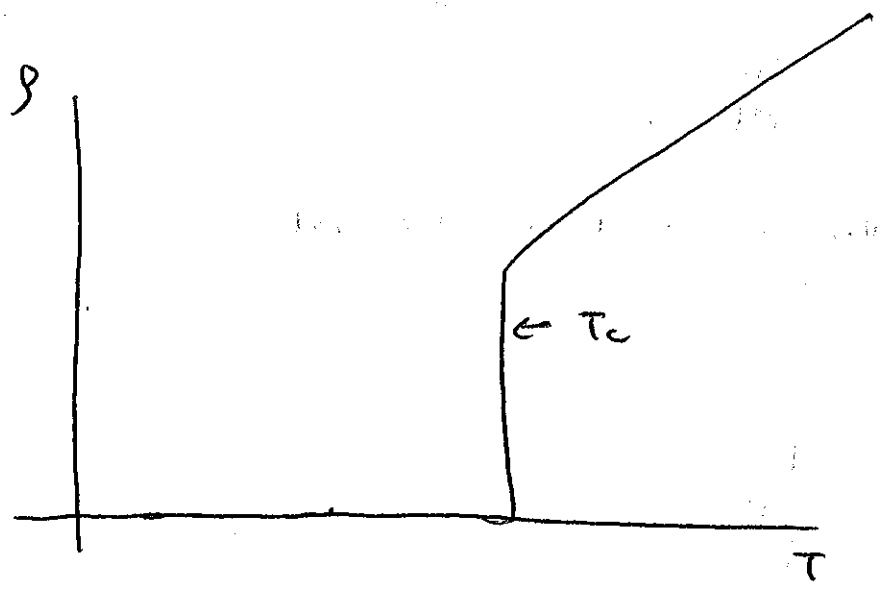

$T_c = 134K$ $HgBa_2Ca_2Cu_3O_8$

Zn 0.85K

Nb 9.46K

$R=0$


WED?

ELECTRICAL POWER

ENERGY J : JOULES $W \cdot s$

POWER $\frac{dE}{dt}$

FAST V.S. SLOW MOVING STORAGE

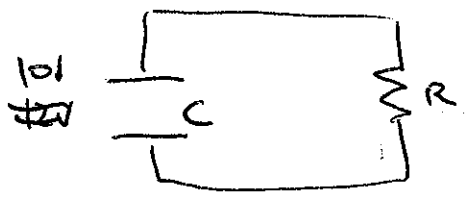


C = 100 μ F

ENERGY STORED

$$\begin{aligned}
 \frac{Q^2}{2C} &= \frac{1}{2} CV^2 = \frac{1}{2} 100 \times 10^{-6} \cdot 10^2 \\
 &= \frac{10^{-2}}{2} \cdot 100 = \frac{1}{2} 10^{-2} \\
 &= 0.5 \times 10^{-2} \text{ J} \\
 &= \boxed{5 \text{ mJ}}
 \end{aligned}$$


ENERGY IN CAPACITOR

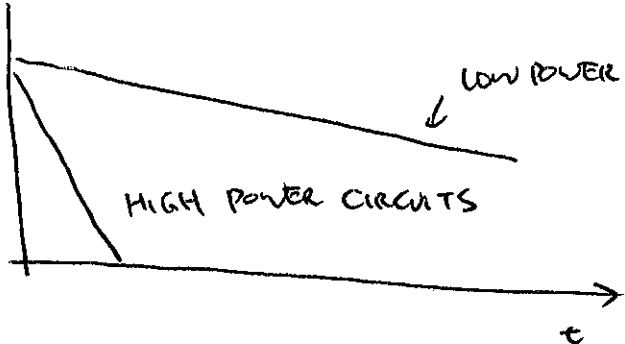

POWER


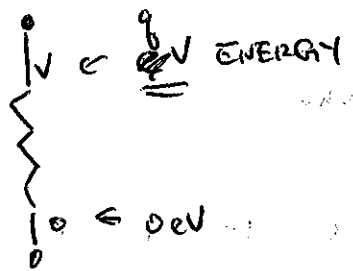
$$I = \frac{V}{R} = \frac{dq}{dt} \quad \# \text{ OF CHARGE PER UNIT TIME}$$



ENERGY DISSIPATED

$$= qV$$

∴ POWER ENERGY DISSIPATED PER UNIT

$$P = \frac{dE}{dt} = \frac{d}{dt} (qV)$$

$$= V \frac{dq}{dt}$$

$$P = IV$$

EXAMPLE.

120V ACROSS 8Ω

$$I = \frac{120V}{8\Omega} = 15A$$

$$P = 15A \cdot 120V = 1800W = \underline{1.8kW}$$

8 BATTERIES 4K Wh

IF SOMETHING TAKES 1000W TO RUN

IT TAKES 4 HRS TO GO EMPTY

EXAMPLE


ELECTRO MOTIVE FORCE : MAX VOLTAGE BATTERIES CAN PROVIDE

INTERNAL RESISTANCE : RESISTANCE WITHIN BATTERY

$$\Delta V = E - I r$$

E : OPEN CIRCUIT VOLTAGE

R : LOAD RESISTANCE

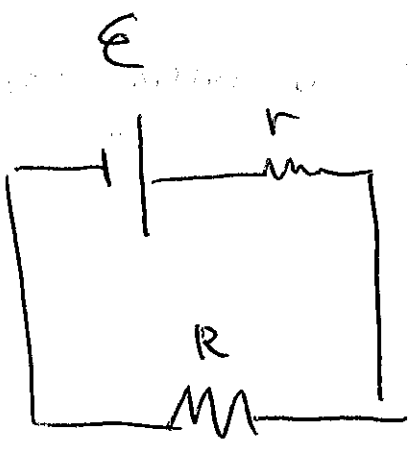

$$I = \frac{E}{R + r}$$

$\frac{1}{2}$

$$P = I^2 R + I^2 r = \text{POWER DELIVERED}$$

$I =$

FOR EXAMPLE

A BATTERY CAN HAVE EMF OF 12V AND INTERNAL RESISTANCE OF 0.05Ω LOAD RESISTANCE IS 3.0Ω

a) FIND CURRENT

$$\frac{12}{3.05\Omega} = 3.93A$$

b) POWER DELIVERED TO THE RESISTOR

$$I^2R = (3.93A)^2 \cdot 3.0\Omega = 46.3W$$

POWER DELIVERED TO THE INTERNAL RESISTOR

$$I^2R_i = (3.93A)^2 \cdot 0.05\Omega = 0.772W$$


TOTAL POWER

$$46.3W + 0.772W = 47.1W$$

FIND R FOR WHICH THE MAX POWER IS
DELIVERED
TO THE LOAD

$$I = \frac{E}{R+r}$$

$$P = I^2 R = \frac{E^2}{(R+r)^2} R$$

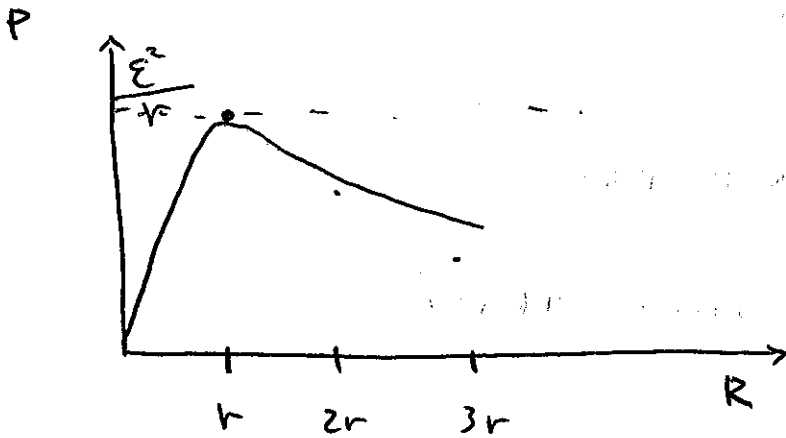

$$\frac{dP}{dR} = \frac{E^2}{(R+r)^2} - \frac{2E^2 R}{(R+r)^3}$$


$$= E^2 \frac{1}{(R+r)^3} [R+r - 2R] = 0$$

$$E \frac{[-R+r]}{(R+r)^3} = 0$$


$$\boxed{R=r}$$

RESISTORS IN PARALLEL AND SERIES

~~(KIRCHOFF'S RULES)~~

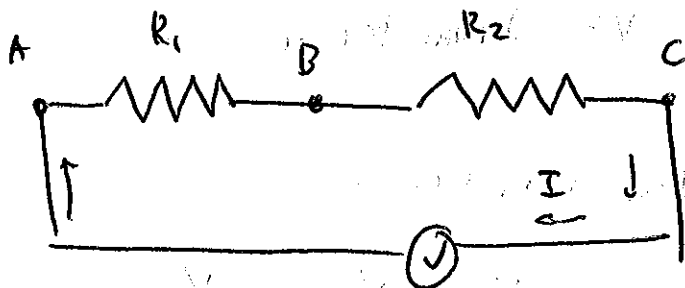


~~$I R$~~ $I R_{TOTAL} = V$

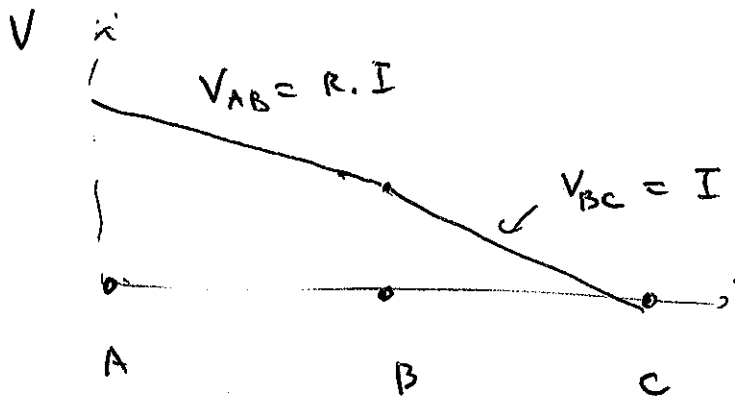

$$V_{AB} + V_{BC} = V = I(R_1 + R_2)$$

$$R_{TOTAL} = R_1 + R_2$$

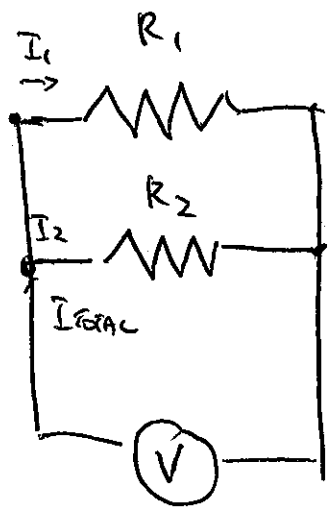

$$V = I_1 R_1$$

$$V = I_2 R_2$$


$$V = I_{TOTAL} R_{TOTAL}$$

$$I_{TOTAL} = I_1 + I_2$$

$$= \frac{V}{R_1} + \frac{V}{R_2} = \frac{V}{R_{TOTAL}}$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

EXAMPLE

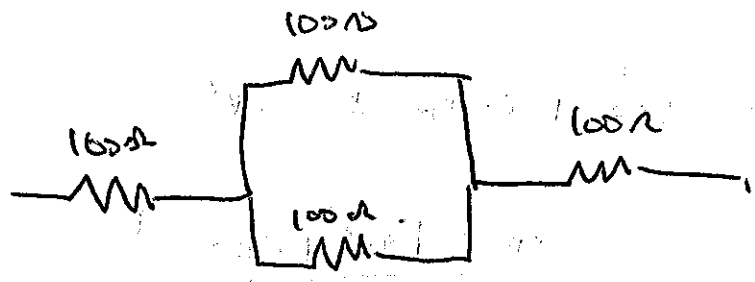


$$\frac{1}{100} + \frac{1}{100} = \frac{1}{R_{ST}}$$

$$R_{ST} = 50\Omega$$


250Ω

WHAT ABOUT

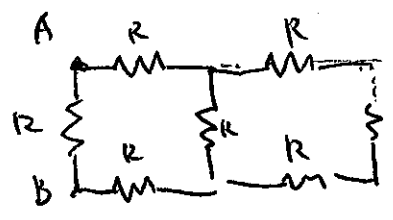

$R_{AB}?$
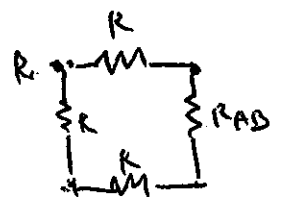
$$\frac{1}{R_{AB}} = \frac{1}{R} + \frac{1}{2R + R_{AB}}$$



$$\frac{1}{R_{AB}} = \frac{2R + R_{AB} + R}{R(2R + R_{AB})}$$

$$\frac{1}{R_{AB}} = \frac{3R + R_{AB}}{2R^2 + R_{AB}R}$$

$$2R^2 + RABR = 3R^2RAB + RAB^2$$

$$0 = RAB^2 + 2R^2RAB - 3R^2RAB - RAB^2$$

$$RAB = \frac{-2R^2 \pm \sqrt{4R^4 + 8R^4}}{2}$$

$$= -R \pm \sqrt{3}R$$

$$\boxed{= R(\sqrt{3} - 1)}$$


EXAMPLE .

FIND EQUIVALENT RESISTANCE



$$\frac{1}{3} + \frac{1}{3} + \frac{1}{3} = \frac{1}{R_{eq}}$$


$$R_{eq} = 1 \Omega$$

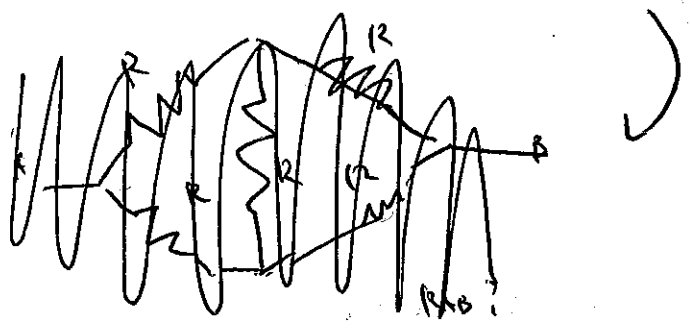

KIRKOFF'S RULES

1. JUNCTION RULES


$$\sum I = 0$$

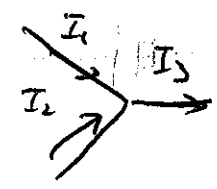

$$I_1 + I_2 - I_3 = 0$$


2. LOOP RULE SUM OF POTENTIAL DIFFERENCES ACROSS ALL ELEMENTS AROUND ANY CLOSED CIRCUITS MUST BE ZERO

119

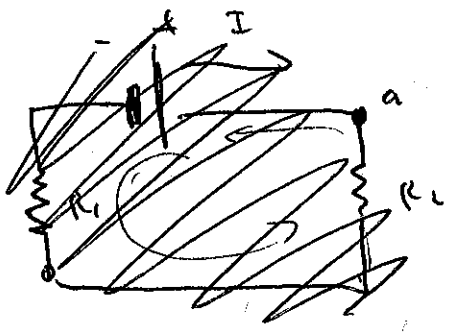

~~WR~~

WHAT DOES IT MEAN?

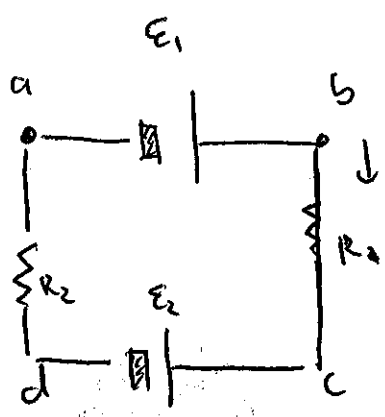


- a → b + E₁
- b → c - IR₁
- c → d - E₂
- d → a - IR₂

$$E_1 - E_2 - IR_1 - IR_2 = 0$$

... ..

EXAMPLE

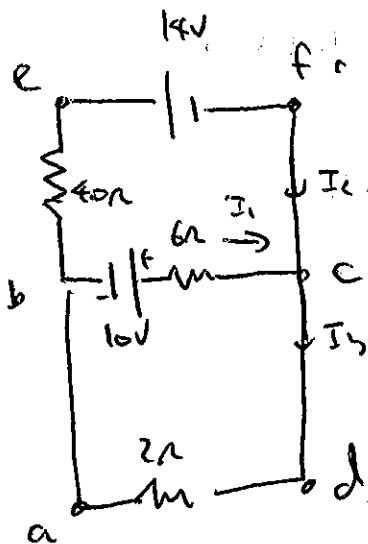


FIND I_1, I_2, I_3

$I_1 + I_2 - I_3 = 0$ KIRCHOFF'S LAW

$abcd = 0 + 10V - I_1 \cdot 6\Omega - I_3 \cdot 2\Omega = 0$


$befcb = -I_2 \cdot 4 - 14V + 6I_1 - 10V = 0$

SUPER POSITION LIVES

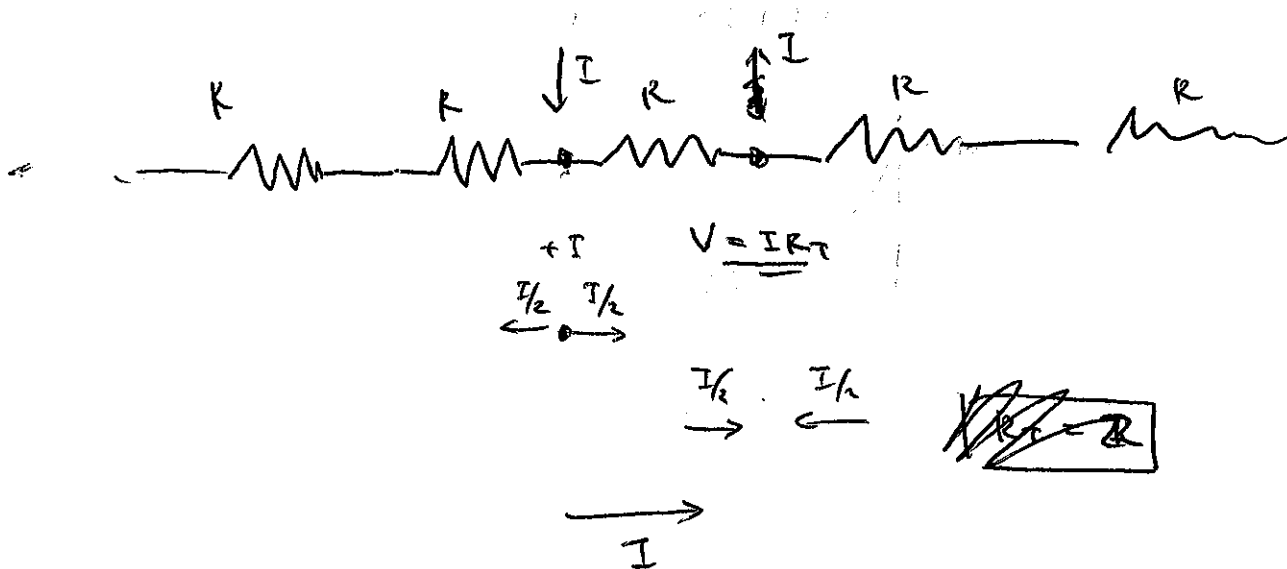

RC CIRCUITS

CAPACITOR

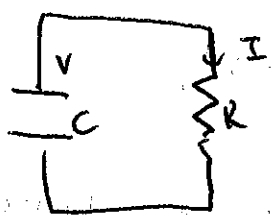

$V(t)$ $Q(t)$

$$\frac{dQ}{dt} = I(t)$$


$$I = \frac{V(t)}{R}$$


$$Q = CV$$

$$C \frac{dV}{dt} = \frac{V(t)}{R}$$

$$\frac{dV}{dt} = \frac{V}{RC}$$

$$V(t) = e^{-\frac{t}{RC}}$$

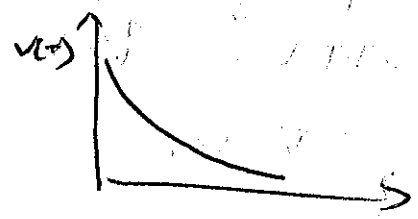

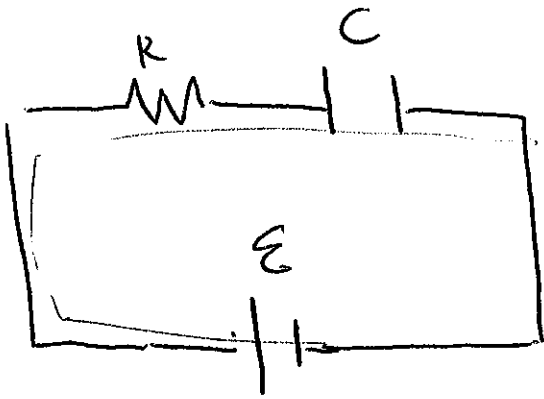

KIRCHHOFF'S LAW

$$\epsilon - \cancel{IR} - \frac{q}{C} = 0$$


$$\epsilon - \frac{dq}{dt}R - \frac{q}{C} = 0$$

$$\frac{dq}{dt} = \frac{\epsilon}{R} - \frac{q}{RC}$$

$$I = \frac{\epsilon C - q}{RC}$$

$$q(t) = C\epsilon (1 - e^{-t/RC})$$

$$\tau = RC$$

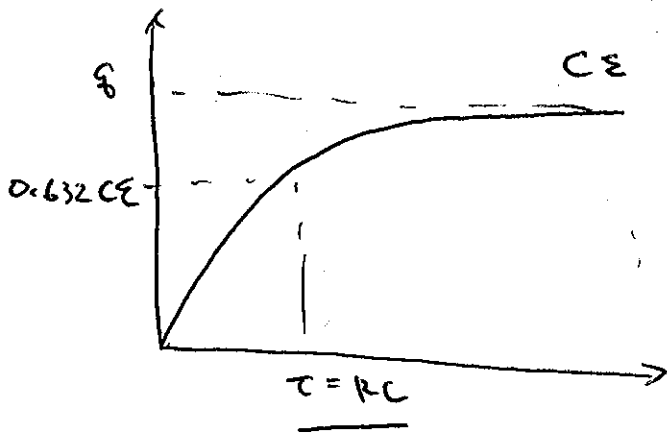

$\tau = RC$

$\frac{dQ}{dt} = \frac{Q}{RC}$
 $\frac{dQ}{Q} = \frac{dt}{RC}$
 $\ln Q = \frac{t}{RC} + \ln C$
 $Q = C e^{\frac{t}{RC}}$

MONDAY EM 367 OHM'S LAW

WED EM 373 LIGHT BULBS, EM 361 HAND BATTERY

FRIDAY EM 382 DISCHARGE THRU A VOLTMETER

(...)