

REVIEW LECTURE

EXAM COVERS FOLLOWING MATERIALS


- DIELECTRICS
- ENERGY IN CAPACITOR
- RESISTANCE, CURRENT, CIRCUITS
 - KIRCHHOFF'S LAW
- MAGNETIC FIELD
 - FORCE ON MOVING CHARGE, FORCE ON WIRE

DIELECTRICS

DIELECTRIC CONSTANT K


INCREASES CAPACITANCE BY FACTOR OF K

EXAMPLE

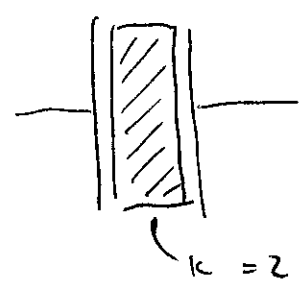

$$\underline{C_{DIE} = C_0 \times 2}$$

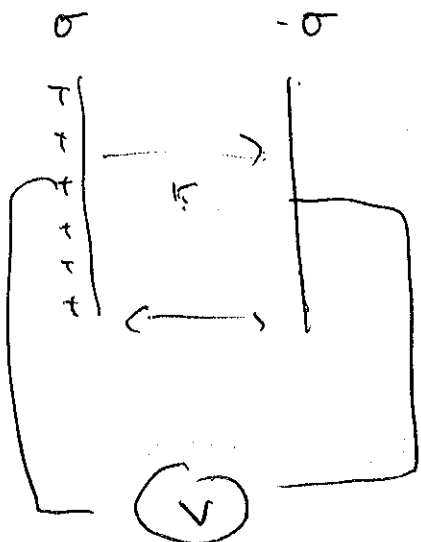ELECTRIC FIELD INSIDE IS
 REDUCED BY
FACTOR OF 2



$$E_{\text{INSIDE}} = \frac{\sigma}{2\epsilon_0}$$

$$V = \frac{\sigma d}{2\epsilon_0}$$


$$Q = CV$$

$$dA = \frac{\sigma d}{2\epsilon_0} C$$

$$\frac{2\epsilon_0 A}{d} = C$$


WHICH IS A FACTOR OF 2 LARGER

ENERGY STORED IN CAPACITOR

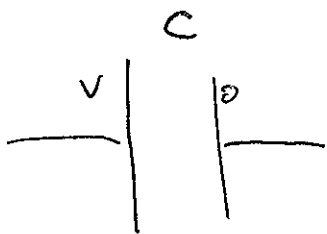


$$\frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}$$

CAPACITORS IN PARALLEL OR SERIES

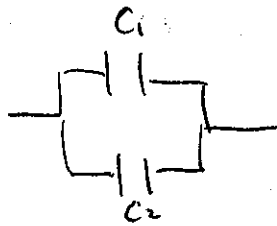



$$C_T = C_1 + C_2$$

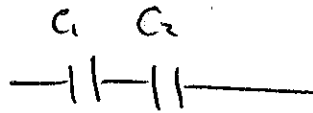

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$$

CAPACITANCE CALCULATIONS

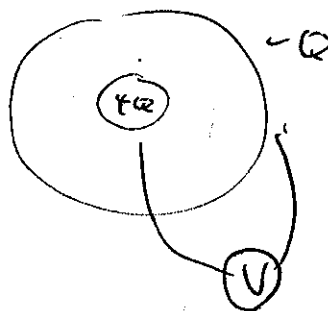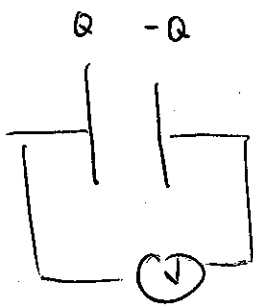CAPACITANCE MEANS IF YOU PUT VOLTAGE U ACROSS IT YOU MOVE EXACTLY Q TO CREATE IT



$CV = Q$ ALWAYS

CIRCUITS

KIRCHHOFF'S RULES AND RESISTANCE & RESISTIVITY

ρ : RESISTIVITY $\Omega \cdot m$


$R = \frac{\rho l}{A} : \Omega$

$\sigma = \frac{1}{\rho}$

GIVEN A WIRE

RESISTANCE DROPS IF AREA IS INCREASED
AND INCREASES IF LENGTH IS INCREASED



KIRCHHOFF'S RULE

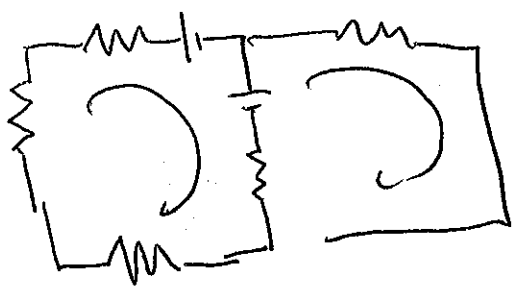

1) VOLTAGE DROP
ACROSS THE ENTIRE
LOOP MUST EQUAL TO
ZER

2) CURRENT MUST BE CONSERVED

TIME DEPENDENT VOLTAGE IN CIRCUITS

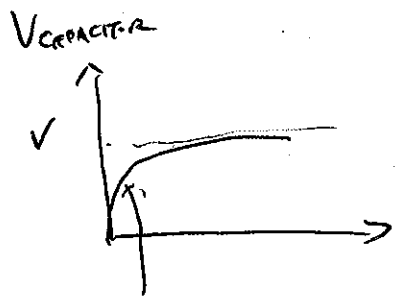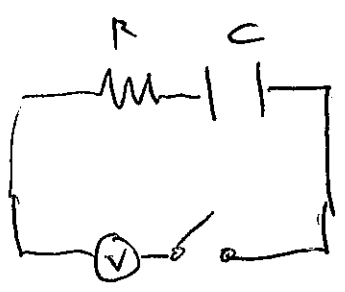


$$V(t) \sim V e^{-\frac{t}{RC}}$$

$$V_0 - V_0 e^{-\frac{t}{RC}}$$


TIME CONSTANT IS ~~THE~~ $\tau = RC$.

$$\tau = 2.73$$

THINK ABOUT THIS

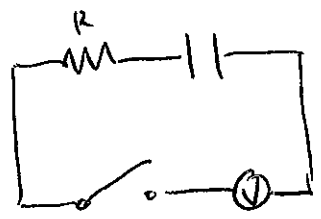

AT $t=0$

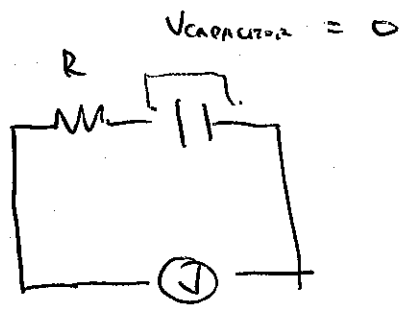


CAPACITOR LOOKS LIKE A SHORT-CIRCUIT

$$V_{RESISTOR} = V$$

$$I = V/R$$

AT $t = \infty$

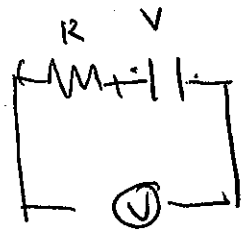

$$V_{RESISTOR} = 0$$

$$I = 0$$

CAPACITOR LOOKS LIKE OPEN CIRCUIT.

MAGNETIC FIELD

$$1 \text{ TESLA} = 10000 \text{ GAUSS}$$

$$\text{EARTH} \sim 0.5 \text{ GAUSS}$$

$$\vec{F}_B = q \vec{v} \times \vec{B}$$

WE ALSO SAY

$$I = q v_d n = n q v_d$$

$$\vec{F}_B = I \vec{L} \times \vec{B}$$

$$\text{OR}$$

$$= \underline{\underline{I \times B}}$$


RIGHT HAND RULE IS REQUIRED

HERE

DIRECTION OF CURRENT:




which way?

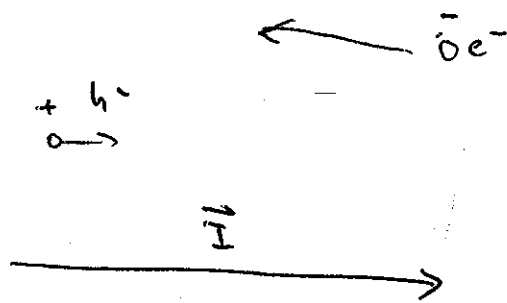

NOTE ON DEPENDENCE.

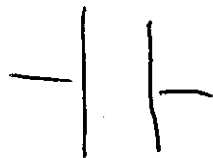EXAMPLE HOW DOES CAPACITANCE DEPENDENT ON AREA IN A PARALLEL PLATE CAPACITOR



EXACT: $C = \frac{\epsilon_0 A}{d}$

$C \sim A$

DEPENDENCE OF RESISTANCE ON LENGTH OF THE WIRE

$R \sim l$

EXTRA

How to MEASURE RESISTANCE
VOLT METER, AMMETER

How TO MEASURE VOLTAGE?

