

**Exam 2 2049H Spring 2009**

*Somas*

**Name:**

**Scores: 1**

**2**

**3**


**4**

**5**

**Total:**

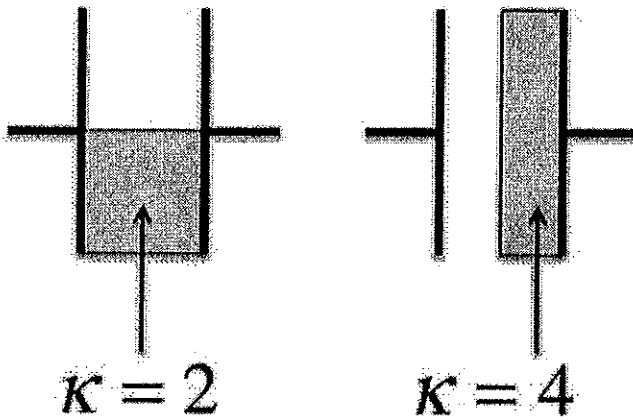**Problem 1 (15 points)**

Parallel capacitors are half filled by dielectric materials as shown below. (a) calculate the capacitances in terms of  $\epsilon_0$ ,  $A$ ,  $d$ . (b) Which capacitor has higher capacitance?




b) RIGHT CAPACITOR HAS HIGHER CAPACITANCE

a)  $C = \frac{\epsilon_0 K A}{2d}$  PARALLEL

$C = \frac{\epsilon_0 A \cdot 2}{2d}$

$C_T = \frac{\epsilon_0 A}{2d} + \frac{\epsilon_0 A}{d}$

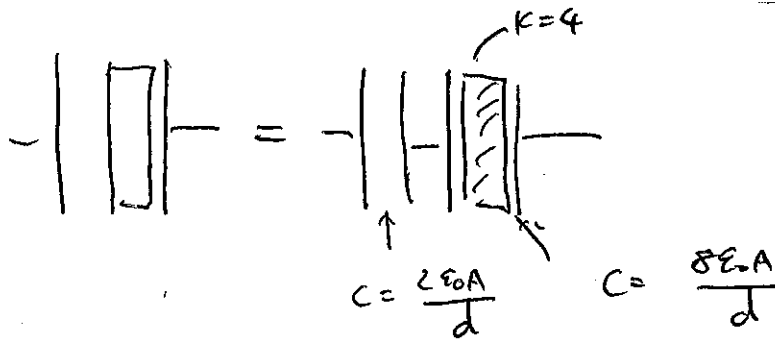$C_T = \frac{3}{2} \frac{\epsilon_0 A}{d} = 1.5 \frac{\epsilon_0 A}{d}$




$\frac{1}{C_T} = \frac{1}{\frac{2\epsilon_0 A}{d}} + \frac{1}{\frac{4\epsilon_0 A}{d}}$

$= \frac{1}{2} \frac{d}{\epsilon_0 A} \left[ \frac{1}{2} + \frac{1}{4} \right] = \frac{d}{\epsilon_0 A} \left[ \frac{3}{4} \right]$

$C_T = \frac{4}{3} \frac{\epsilon_0 A}{d} = 1.33 \frac{\epsilon_0 A}{d}$

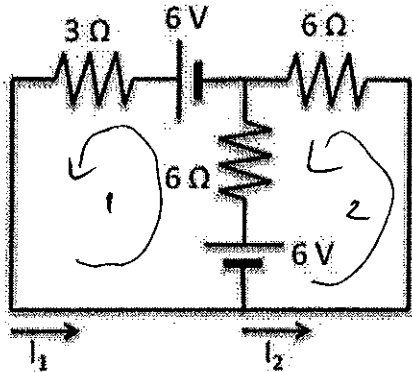Problem 2 (20 points)

Calculate  $I_1$  and  $I_2$  for the circuit shown left.



$$12 \sqrt{-\frac{27}{2} + \frac{43}{42}}$$

Loop 1  $\Delta V = 6V - 6(I_1 - I_2) + 6 - 3I_1$   
 $= 12 - 6I_1 + 6I_2 - 3I_1$   
 $= 12 - 9I_1 + 6I_2 = 0 \dots (1)$

Loop 2  $\Delta V = -6I_2 - 6(I_2 - I_1) = 6 = 0$   
 $-12I_2 + 6I_1 = 6 \dots (2)$

(1) :  $12 = 9I_1 - 6I_2$

(2) :  $6 = 6I_1 - 12I_2$

(2)  $\times \frac{3}{2}$  ;  $9 = 9I_1 - 18I_2$  ; (3)

(1) - (3)  $\Rightarrow$   $3 = 0 + 12I_2$

$$\boxed{I_2 = \frac{1}{4} A}$$


PLUG BACK INTO (2)

$$\boxed{I_1 = \frac{3}{2} A}$$

$$-3 + 6I_1 = 6$$

$$6I_1 = 9$$

**Problem 3 (30 points)**

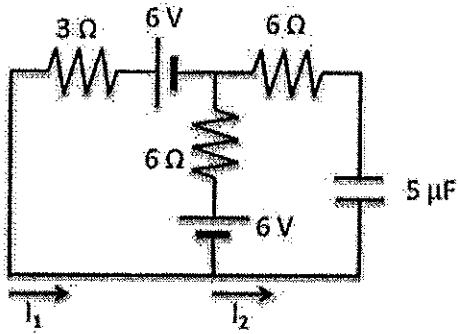


(a) Calculate  $I_1$  in the steady state ( $t = \infty$ ). Note that at this point  $I_2$  should be equal to zero.

(b) Calculate the charge stored in the capacitor in the following circuit.

(c) What is the characteristic charging time (the RC time constant) for the capacitor?

a) IF  $I_2 = 0$  CIRCUIT LOOK LIKE

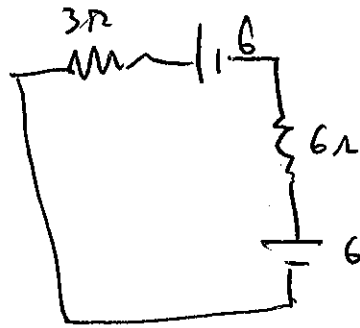


$$6 - 6I_1 + 6 - 3I_1 = 0$$

$$12 = 9I_1$$

$$\frac{4}{3} = I_1$$


$$I_1 = \frac{4}{3} \text{ A}$$

b) IF  $I_1 = \frac{4}{3}$

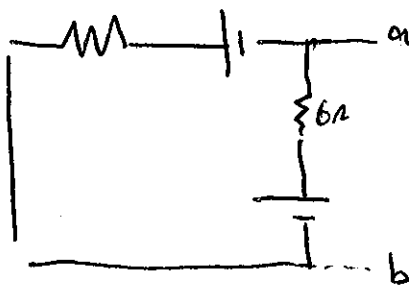

$$V_{ab} = -\frac{4}{3} \cdot 6 + 6$$

$$= -2 \text{ Volts}$$

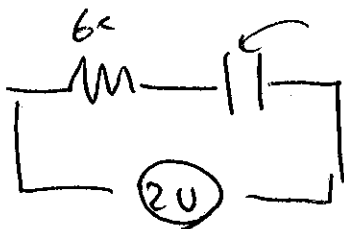

$$V_{\text{CAPACITOR}} = 2 \text{ V}$$

$$CV = Q$$

$$5 \times 10^{-6} \cdot 2 \text{ V} = Q = 1 \times 10^{-5} \text{ C}$$

c) RC TIME CONSTANT IS


$$R = 6\Omega$$

$$C = 5\mu F$$



$$RC = (6\Omega)(5\mu F) = 30 \times 10^{-6} \text{ sec}$$

$$= \boxed{30 \mu s}$$

Problem 4 (20 points)

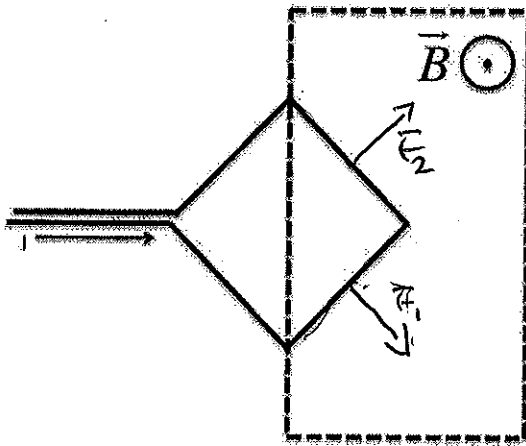

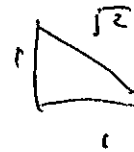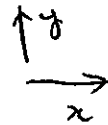Calculate the force due to magnetic field on a wire which has been shaped into a square shape as shown left. The square has sides of 1 m, the magnetic field is 0.1 T, and the current is 1 A. Magnetic field is only present in the dotted square as indicated in the figure.




$$|\vec{F}_1| = |\vec{F}_2| = |I \vec{L} \times \vec{B}| = 1 \text{ A} \cdot 1 \text{ m} \cdot 0.1 \text{ T} = \boxed{0.1 \text{ N}}$$

BUT FORCES IN y DIRECTION CANCEL AND ONLY FORCES IN x DIRECTION ADD

$$F_T = 0.1 \text{ N} \cdot \frac{2}{\sqrt{2}} = 0.1 \frac{\sqrt{2}}{1} = \boxed{0.141 \text{ N}} \text{ IN X DIRECTION}$$

Problem 5 (15 points)

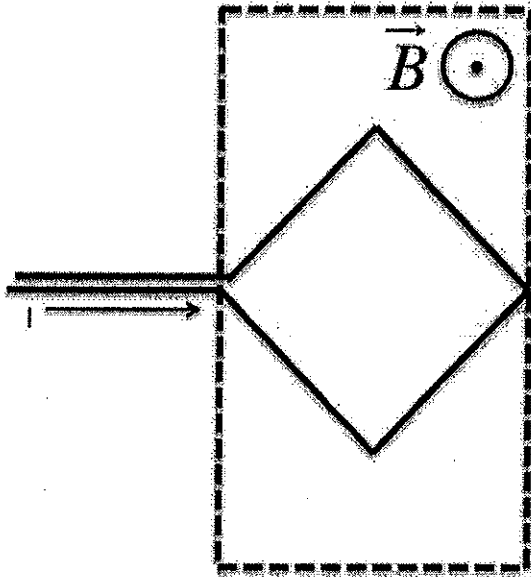

Calculate the force if the metal square has been inserted further into the magnetic field. Everything else remains the same. The square has sides of 1 m, the magnetic field is 0.1 T, and the current is 1 A. Magnetic field is only present in the dotted square as indicated in the figure.



ALL FORCES CANCEL

$$F = 0$$